


3/24/2015

## Chapter 7 - Inductors + Capacitors


- Capacitors  $C$  + Inductors  $L$
  - $L$ 's +  $C$ 's can store + deliver infinite amounts of energy.
- Move into the realm of active vs. passive elements.  
Active elements supply energy and can supply an average power greater than  $\emptyset$  over an infinite time interval

**Capacitors**  $C$  is defined by a  $V$ - $I$  relationship  
 where  $i = C \frac{dv}{dt}$   $v$  and  $i$  are functions of time!  
 Capacitance is an ampere-second per volt, or coulomb per volt  
 which is equivalent to one Farad (F)  $\frac{\text{Coulomb}}{\text{Volt}}$

$$i = C \frac{dv}{dt} \Rightarrow dv = \frac{i dt}{C}$$


$i = \frac{dq}{dt}$  change in charge on plate over time

$$C = \frac{\epsilon A}{d}$$

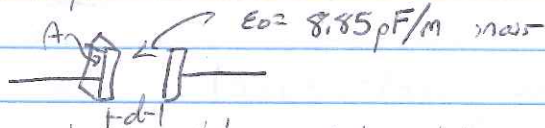

two parallel conducting plates  
 plates have area  $A$  separated by insulating  
 conductor w/  $\epsilon = \text{permittivity}$   
 separated by distance  $d$ .

CoF several hundred  $\mu\text{F}$  is very large

**Example 7.1**  $i = C \frac{dv}{dt}$  a)  $i = 2 \times 5 \frac{dv}{dt} = 10A$

b) first waveform is a sine, derivative is a cosine,  
 multiplied by 2 w/ same frequency.

**Practice 7.1**

Determine  $I$  if  $v = 2e^{-5t} \text{ V}$  w/  $C = 5 \text{ mF}$

$$I = C \frac{dv}{dt} = 5 \times 10^{-3} \times 2e^{-5t} \frac{d}{dt} = -5 \times 5 \times 10^{-3} \times 2e^{-5t} = -50e^{-5t} \text{ mA} = i(t)$$

$$i(t) = C \frac{dv}{dt} \Rightarrow dv(t) = \frac{1}{C} i(t) dt$$

Integrate both sides between  $t_0$  to  $t$

we get

$$\int_{v(t_0)}^{v(t)} dv = \frac{1}{C} \int_{t_0}^t i(t') dt'$$

$$= v(t) - v(t_0) = \frac{1}{C} \int_{t_0}^t i(t') dt'$$

$$\therefore v(t) = \frac{1}{C} \int_{t_0}^t i(t') dt' + v(t_0) \quad \text{or } v(t) = \frac{1}{C} \int i dt + K$$


In many cases  $v(t_0)$  is not discernable + usually

such that  $t_0 = -\infty + v(-\infty) = 0$

$$v(t) = \frac{1}{C} \int_{-\infty}^t i dt'$$

Again  $q(t) = C v(t)$

Example 7.2

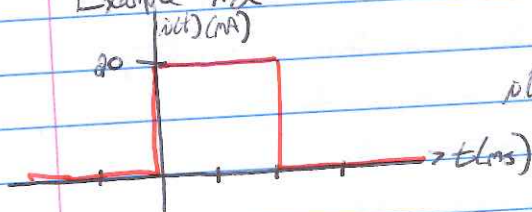

solve over intervals

$$i(t) = \begin{cases} 0 & -\infty \leq t < 0 \\ 20 \text{ mA} & 0 \leq t < 2 \text{ ms} \\ 0 & 2 \text{ ms} \leq t < \infty \end{cases}$$

Interval (1)  $i(t_0) = 0 \Rightarrow v(t_0) = 0$

$$(2) \quad v(t) = \frac{1}{C} \int_{t_0}^t i(t') dt' + v(t_0)$$

$$v(t) = \begin{cases} 0 & -\infty \leq t < 0 \\ 4000 t & 0 \leq t < 2 \text{ ms} \end{cases}$$

Because  $i(t_0) = 0 \Rightarrow v(t_0) = 0$


$$\frac{1}{5 \mu\text{F}} \int_0^{2 \text{ ms}} 20 \text{ mA} dt = \frac{1}{5 \times 10^{-6}} \times 20 \times 10^{-3} \cdot t$$

$$= v(t) = 4000 t \quad 0 \leq t < 2 \text{ ms}$$

Interval (3)

$$v(t_0) = v(2 \text{ ms}) = 4000 \times 2 \text{ ms} = 8 \text{ V} \quad v \geq 2 \text{ ms} = 0$$
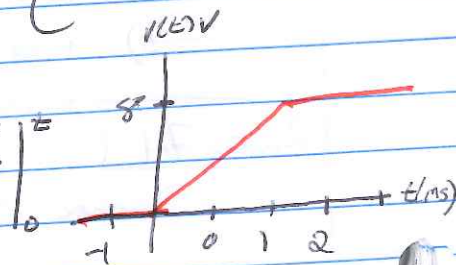
$$\therefore v(t) \text{ for } t \geq \infty = 8 \text{ V} + 0 = 8 \text{ V}$$



Energy Storage  $p = v \cdot i = C v \frac{dv}{dt} \Rightarrow p dt = C v dv$

Change in Energy over time:  $\int_{t_0}^t p dt = C \int_{v(t_0)}^{v(t)} v' dv'$

$p = \frac{dE}{dt}$   $\int p = \text{Energy}$

$$= \left[ \frac{v(t)^2}{2} - \frac{v(t_0)^2}{2} \right] \cdot C$$

$w_c(t) - w_c(t_0) = \frac{C}{2} \left\{ [v(t)]^2 - [v(t_0)]^2 \right\}$

If Energy at  $t_0 = 0$  then we have

$$w_c(t) = \frac{1}{2} C v^2$$

### Ideal Capacitor

\* No current if voltage is not changing with time

Open circuit to DC

\* Finite amount of energy can be stored across the capacitor (current zero, voltage constant)

\* Capacitor cannot change voltage instantaneously, but current through can

\* Stores energy does not dissipate energy.

### Inductor

$L$  is also defined by a voltage-current relationship

$$v = L \frac{di}{dt}$$

$\frac{v}{i} \rightarrow L$   
 Henry (H)  
 volt-second per ampere

Inductor is realized by winding a wire into a coil.


where inductance is determined by  $\mu N^2 A / s$

$N$ : # of complete turns of wire

$A$ : is cross section area

$s$ : is the axial length of the helix

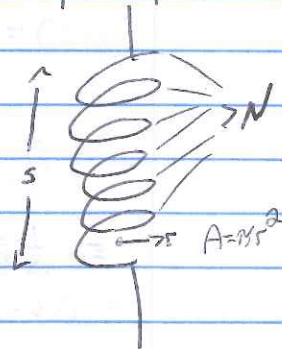$\mu$  is material permeability.  $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$



Voltage across an inductor is related to time rate of change of the current through it

no voltage across an inductor yields a short circuit ~~when~~ when current is constant

Instantaneous changes in voltage is possible, but NOT current through an inductor

Example 7.4  $v = L \frac{di}{dt}$

$$\therefore di = \frac{1}{L} v dt$$

$$\int_{i(t_0)}^{i(t)} di' = \frac{1}{L} \int_{t_0}^t v(t') dt'$$

$$i(t) - i(t_0) = \frac{1}{L} \int_{t_0}^t v dt'$$

$$\hookrightarrow i(t) = \frac{1}{L} \int_{t_0}^t v dt' + i(t_0)$$

$$\therefore i(t) = \frac{1}{L} \int v dt + k$$

$$\text{if } i(t_0) = i(\infty) = 0, \quad i(t) = \frac{1}{L} \int_{-\infty}^t v dt'$$

Example 7.6  $v(t) = 6 \cos 5t \text{ V}$

$$i(t) = \frac{1}{L} \int_{t_0}^t 6 \cos 5t dt + i(t_0)$$

$$= \frac{1}{2} \int_{t_0}^t 6 \cos 5t dt + i(t_0)$$

$$= \frac{1}{2} \left( \frac{6}{5} \sin 5t - \frac{6}{5} \sin 5(t_0) \right) + i(t_0)$$

$$= 0.6 \sin 5t - 0.6 \sin 5t_0 + i(t_0)$$

plug in  $-\frac{\pi}{2}$  for  $t_0 = (-\frac{\pi}{2})$   $i(t_0) = 1 \text{ A}$

$$\begin{aligned} \therefore i(t) &= 0.06 \sin 5t - 0.06 \sin 5 \cdot \frac{\pi}{2} + 1 \\ &= 0.06 \sin 5t + 1.06 = i(t) \end{aligned}$$

Energy Storage  $P = VI = Li \frac{di}{dt}$

$$\Rightarrow P dt = L i di$$

looking for energy  $w_L$

$$\int_{t_0}^t P dt' = L \int_{i(t_0)}^{i(t)} i' di'$$

$$= w_L(t) - w_L(t_0) = \frac{1}{2} L [i(t)^2 - i(t_0)^2]$$

$$\therefore w_L(t) = \frac{1}{2} L [i(t)^2 - i(t_0)^2] + w_L(t_0)$$

if energy is 0 at time 0,  $w_L(t) = \frac{1}{2} L i^2$

### Ideal Inductor

\* No voltage across inductor if current is not changing w/ time.  
(short-circuit to DC)

\* Finite amount of energy ~~can~~ can be stored in inductor, even if voltage across is zero.

\* Current cannot change instantaneously, voltage can.

\* Inductors do not dissipate energy, they only store it.

### Series + Parallel

- ① L's in series act like R's in series
- ② L's in parallel act like R's in parallel
- ③ C's in series act like R's in parallel
- ④ C's in parallel act like R's in series