

Tuesday Jan 27th 2, Tuesday May 5th

Tuesday 3/31/2015


figs. 275-294

- Review
- Natural Response \rightarrow general nature
 - Transient Response \rightarrow dies out
 - Forced Response \rightarrow steady-state transition

Source Free: $i(t) = I_0 e^{-Rt/L}$


Exponential Response at $t=0$ current = I_0
current decreases as time increases, exponential decay
decay function: $e^{-Rt/L}$

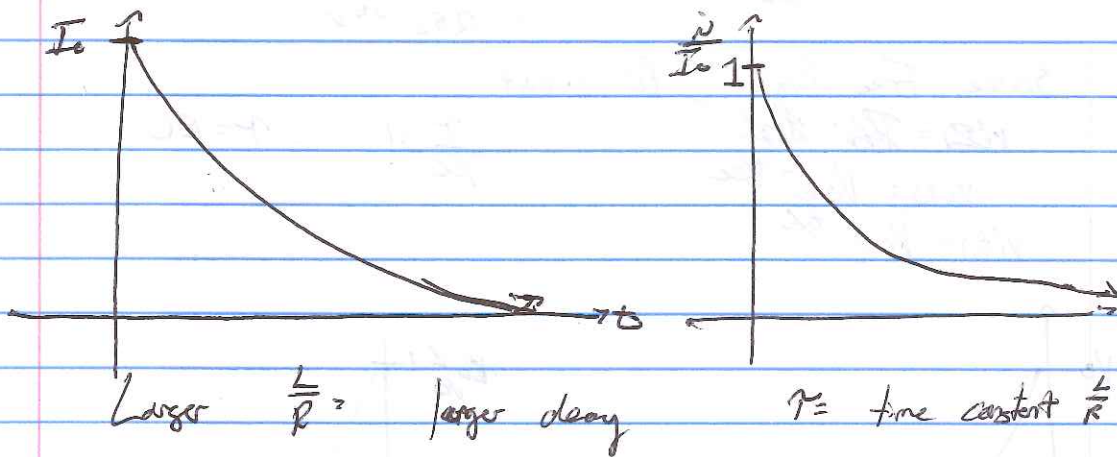Same function for RL Series circuit as long as
 L/R ratio is the same





$\tau = 0.3679s$

$5\tau \sim 6\tau$ negligible current

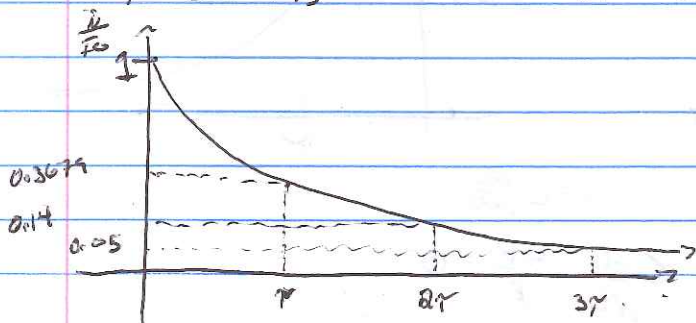

Practice 8.2

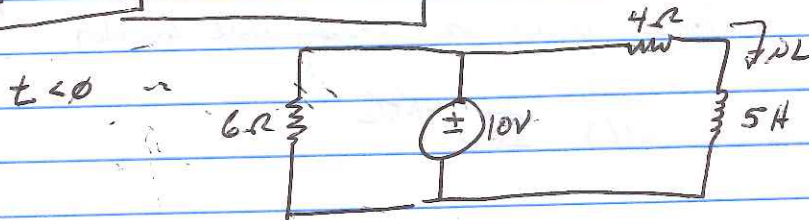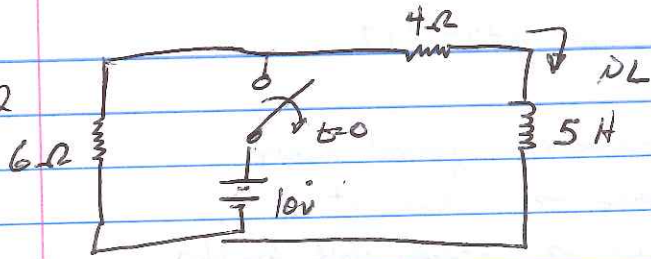

$V = IR$

$$i_L(t=0) = \frac{10V}{R} e^{-\frac{10}{5}t} = \frac{10}{4} = I_0 = 2.5$$




$$i_L(t=0) = 2.5 e^{-2t}$$

$$v_L = L \frac{di}{dt} = (-2)(5)(2.5)e^{-2t} = -2.5e^{-2t} V$$

Source Free Parallel RL circuit

~~$v(t) = I_0 e^{-t/RC}$~~
 $v(t) = V_0 e^{-t/RC}$
 $v(t) = V_0 e^{-t/\tau}$



$\frac{\tau}{RC} = 1 \quad \tau = RC$

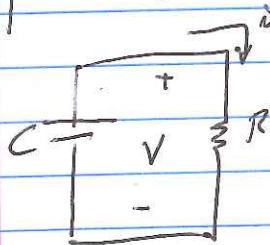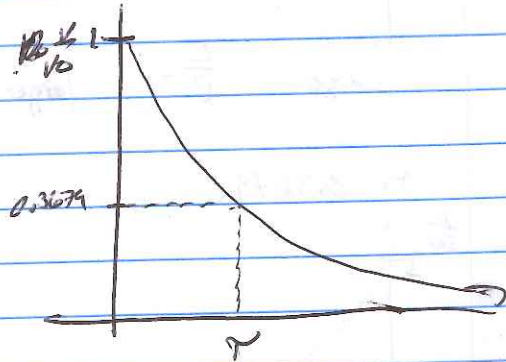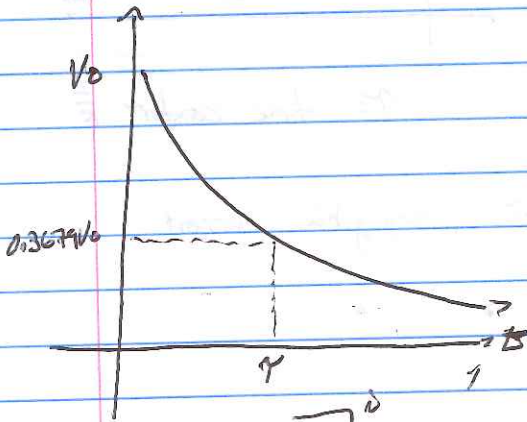

$i = C \frac{dv}{dt}$

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

Example 8.3

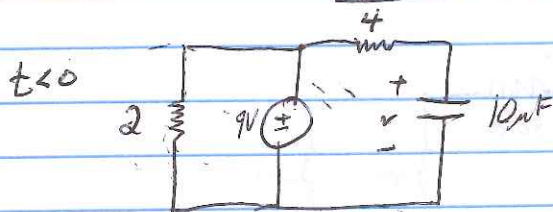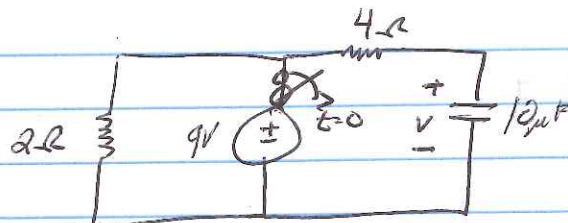


$$V(t < 0) = 9V$$

$$i_{4\Omega}(t < 0) = 0A$$

$$\tau = 6 \times 10^{-6}$$


$$= 60 \times 10^{-6}$$

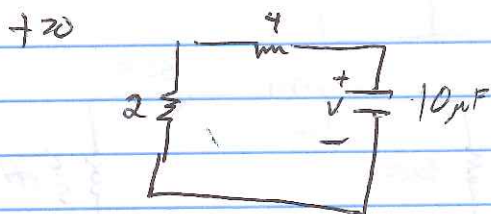

$$V(t) = V_{oc} e^{-t/\tau}$$

$$= V_{oc} e^{-t/RC} V$$

Practice 8.4

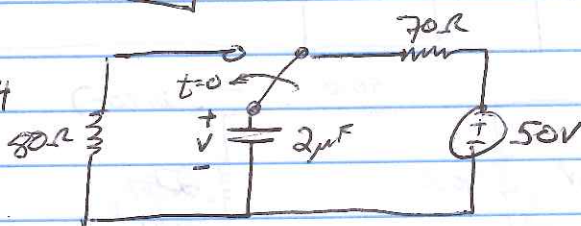

$$V(t > 0) = 50V$$




$$V(t > 0) = 50 e^{-t/RC} \quad V = 50 e^{-t/80\mu s}$$

General Perspective For RL Circuits

$$\tau = \frac{L}{R_{eq}} \rightarrow \tau = \frac{L_{eq}}{R_{eq}}$$

★ Always $i_L(0^-) = i_L(0^+)$ ★

Example 8.4

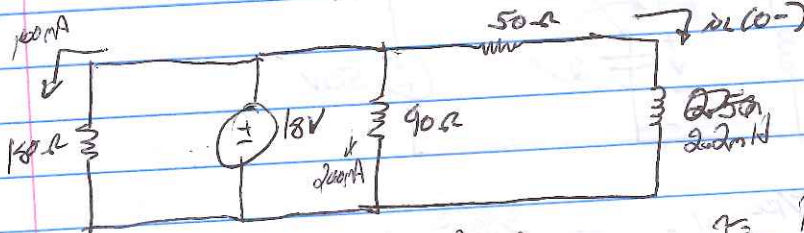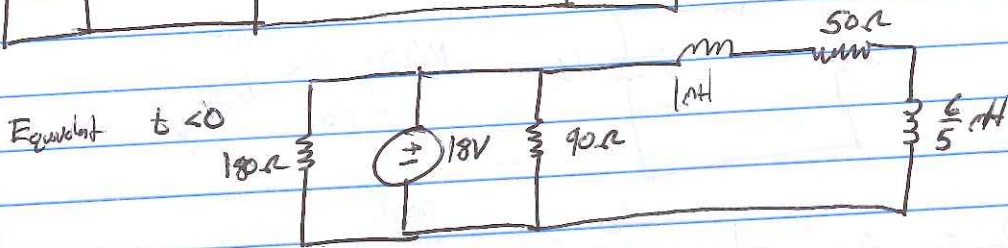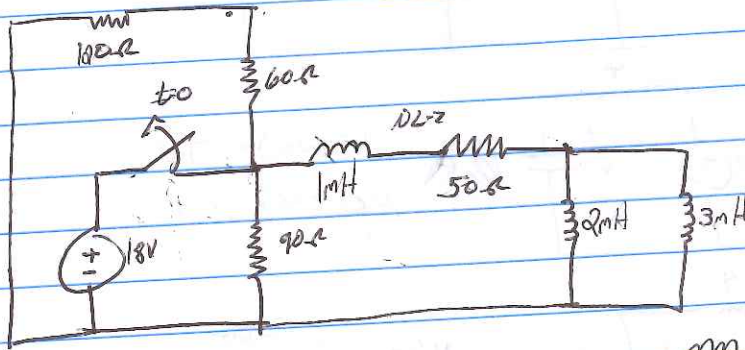

$$i_1(0^-) = \frac{18V}{90\Omega} = 200\mu A$$

$$i_L(0^-) = \frac{18}{50} = 360\mu A$$

$$i_L(0^-) = i_L(0^+) = 360\mu A$$


~~300 = 360 μA~~

$$\tau = \frac{L_{eq}}{R_{eq}} = \frac{60 + 50}{\dots}$$

$$i_1(0^+) = -i_L(0^+) \times \frac{180}{180 + 90} = -240\mu A$$

$$= -360 \times \frac{2}{3} = -120 \times 2 \uparrow$$

Practice

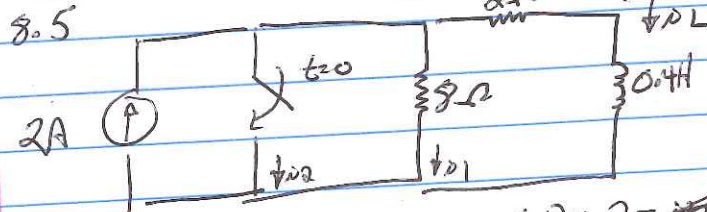

$$\tau = \frac{L}{R} = \frac{0.4}{2} = 0.2$$

$$i_2(0^-) = 0A$$

$$i_1(0^-) = \frac{2}{10} \times 2 = 0.4A$$

$$i_L(0^-) = \frac{8}{10} \times 2 = 1.6A$$

$$i_L(0^+) = 1.6A$$

$$i_2(0^+) = 2 - i_L(0^+) = 2 - 1.6 = 0.4A$$

$$i_L(t) = i_L(0^+) e^{-t/\tau}$$

$$i_2(t) = 2 - i_L(t) = 2 - 1.6 e^{-t/0.2}$$

General RC Circuits

$$\tau = R_{eq} C$$

$$\tau = R_{eq} C$$

$$\tau = R_{eq} C$$

~~Example 2.5~~ Ex 8.5

$$v(t+) = v(t-) = V_0$$

$$R_{eq} = \frac{R_1 R_2 + R_2}{R_1 + R_2}$$


$$v(t) = V_0 e^{-t/\tau}$$

$$\tau = \left(\frac{R_1 R_2 + R_2}{R_1 + R_2} \right) C$$


$$i(t) = i(t-) e^{-t/\tau}$$

mit Step

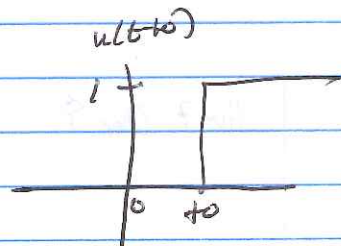
$$u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$$



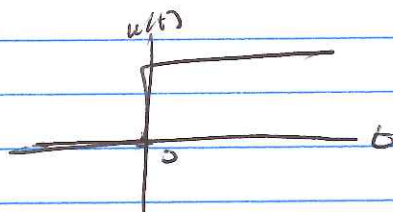
$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t > 0 \end{cases}$$




Rectangular Pulse

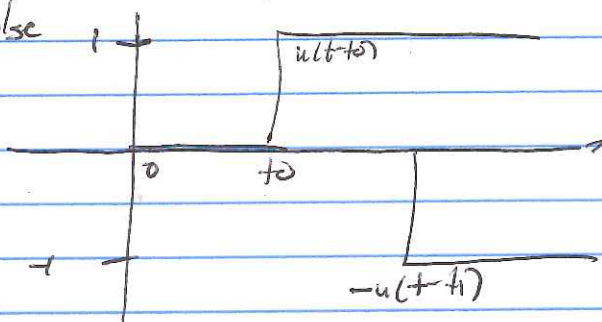
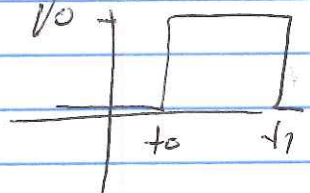
$$v(t) = \begin{cases} 0 & t < t_0 \\ V_0 & t_0 < t < t_1 \\ 0 & t > t_1 \end{cases}$$



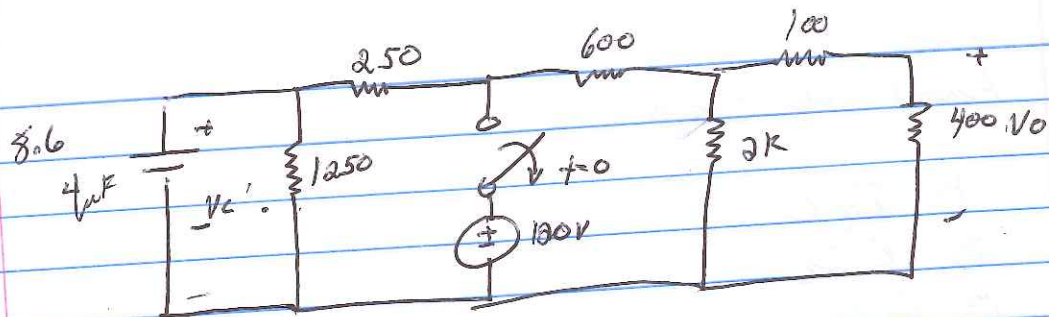

$$V_c(0^-) = 120 \times \frac{1250}{1500} = 100\text{V} = V_c(0^+)$$

$$V_o(0^-) = \frac{2000 \times 500}{2500} = 400$$

$$120 \times \frac{400}{1000} = 48\text{V}$$

$$48 \times \frac{400}{500} = 38.4$$

HW 7 Chap 8 20, 22, 27, 48, 53, 57