

- 20 MCQ - fill in every answer. Do not leave any blanks!
- 3 3.5" x 5" note cards for crib sheets
- No calculators or other materials, bring NYU ID


Chapter 7

Capacitors

$$v = C \frac{dv}{dt}$$

C measured in Farads

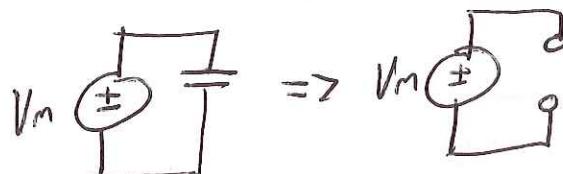DC voltage across a capacitor results in zero current flow (Open Circuit)



A steady state circuit w/ DC source, capacitor acts like open circuit.

Voltage across a capacitor can **NOT** change instantaneously!

Current through a capacitor **can** change instantaneously

$$dv = \frac{1}{C} i(t) dt$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t') dt' + v(t_0)$$


Energy: $w_c(t) = \frac{1}{2} C \left\{ [v(t)]^2 - [v(t_0)]^2 \right\} + w_c(t_0)$

Inductors

$$v = L \frac{di}{dt}$$

L measured in Henrys

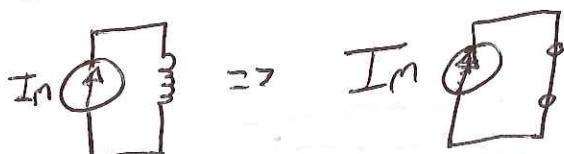DC current flow through an inductor results in zero voltage potential (short circuit)



A steady state circuit w/ DC source, inductor acts like a short circuit

Current through an inductor can **NOT** change instantaneously!

Voltage across an inductor **can** change instantaneously!

Current through (or voltage across) a Resistor ~~can~~ **not** change instantaneously!

$$di = \frac{1}{L} v dt$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v dt' + i_0(t_0)$$

Energy:

$$w_L(t) = \frac{1}{2} L \left\{ [v(t)]^2 - [i(t)]^2 \right\} + w_L(t_0)$$

Series Inductors: $L_{eq} = L_1 + L_2 + \dots + L_N$

Parallel Inductors: $L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N}}$


Series Capacitors: $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N}}$

Parallel Capacitors: $C_{eq} = C_1 + C_2 + \dots + C_N$

Chapter 8

R-L circuit \Rightarrow

Source Free

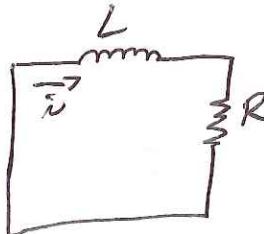

$$0 = Ri + \frac{L di}{dt}$$


$$i(t) = I_0 e^{-Rt/L}$$

$$v_L = I_0 e^{-Rt/L}$$


Source Free w/
some initial current

I_0
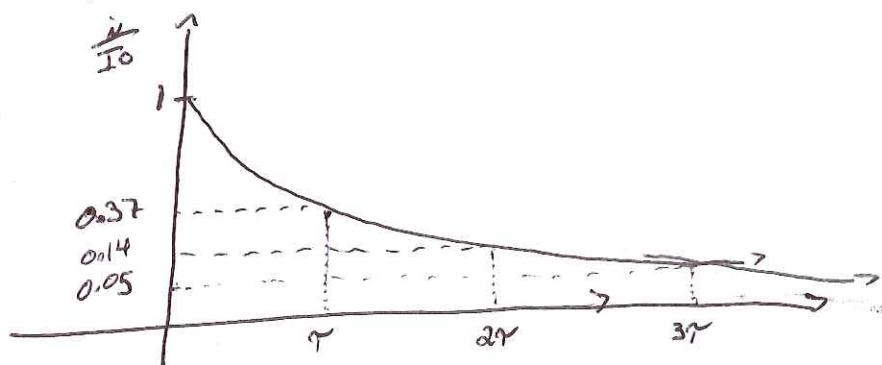
$$\gamma = \frac{R}{L} \text{ in seconds}$$



R-C Circuit \Rightarrow

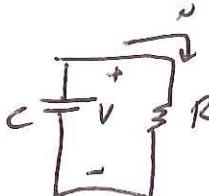

$$C \frac{dv}{dt} + \frac{V}{R} = 0$$

$$v(t) = V_0 e^{-t/RC}$$

Source Free w/ some
initial Voltage V_0

$$\gamma = RC \text{ in seconds}$$




②

$$\gamma = \frac{L_{eq}}{R_{eq}}$$

$$\gamma = R_{eq} C_{eq}$$

Determine γ during the transient state

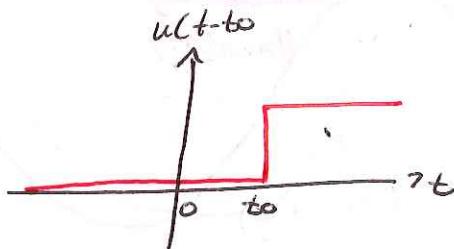unit step function $u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t \geq t_0 \end{cases}$



$$u(t) = \begin{cases} 0 & t < 0 \\ 1 & t \geq 0 \end{cases}$$

Natural + Forced Response.

\hookrightarrow similar to source \hookrightarrow adding a new source to the circuit free

Complete Response = Natural Response + Forced Response

$$D = DN + DF$$

Determine based on initial + final conditions

~~A~~ $\rho_L(0^-) = \rho_L(0^+), \rho_L(\infty)$
~~A~~ $v_C(0^-) = v_C(0^+), v_C(\infty)$

$$f(0^+) = f(\infty) + A; \quad f(t) = f(\infty) + [f(0^+) - f(\infty)]e^{-\gamma t}$$

$$\rho_L(t) = \rho_L(\infty) + [\rho_L(0^+) - \rho_L(\infty)]e^{-\gamma t}$$

$$v_C(t) = v_C(\infty) + [v_C(0^+) - v_C(\infty)]e^{-\gamma t}$$


Chapter 10

$$V(t) = V_m \sin(\omega t)$$

$$f = \frac{1}{T}$$

$$\omega T = 2\pi$$

$$\omega = 2\pi f$$

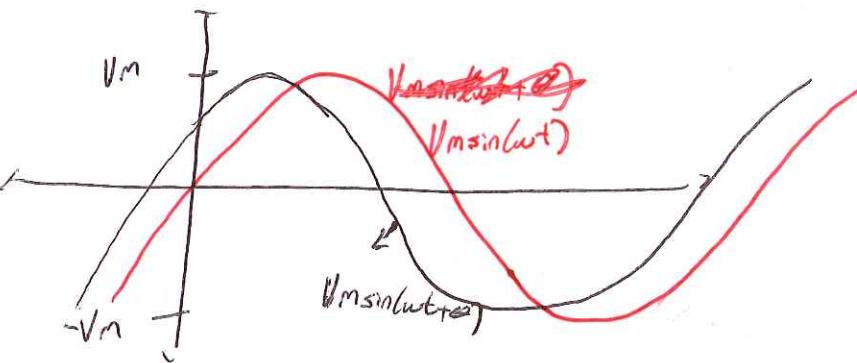

$V_m \sin(\omega t)$ lags $V_m \sin(\omega t + \theta)$ by θ rads

$$-\sin \omega b = \sin (\omega t + 180^\circ)$$

$$-\cos \omega b = \cos (\omega t + 180^\circ)$$

$$\sin(\omega t) = \cos(\omega t - 90^\circ)$$

$$\cos(\omega t) = \sin(\omega t + 90^\circ)$$

can combine terms w/ common frequencies

$$e^{j\theta} = \cos \theta + j \sin \theta$$

Phasors Practice 10.6 $\omega = 2000 \text{ rad/s}$ Find instantaneous current at $t = 1 \text{ ms}$ for

a) $j10A = 10L90^\circ \rightarrow i(0.001) = 10 \cos(2000 \times 0.001 + \frac{\pi}{2})$

b) $20 + j10A \rightarrow 20 \cos(2000 \times 0.001) + j \sin(2000 \times 0.001)$

or $\sqrt{20^2 + 10^2} \neq \tan^{-1}\left(\frac{10}{20}\right) = 22.36 \angle 0.4636 \text{ rads}$
 $= 22.36 \angle 26.56$


$\rightarrow 22.36 \cos(2000 \times 0.001 + 0.4636) + j \sin(2000 \times 0.001 + 0.4636)$

c) $20 + 10L20^\circ = 10 \cos(20^\circ) + j \sin(20^\circ)$


$$\boxed{j^2 = -1}$$

Impedance $Z_R = R$
 $Z_L = j\omega L$
 $Z_C = \frac{1}{j\omega C}$

Chapter 8 Exercise 22

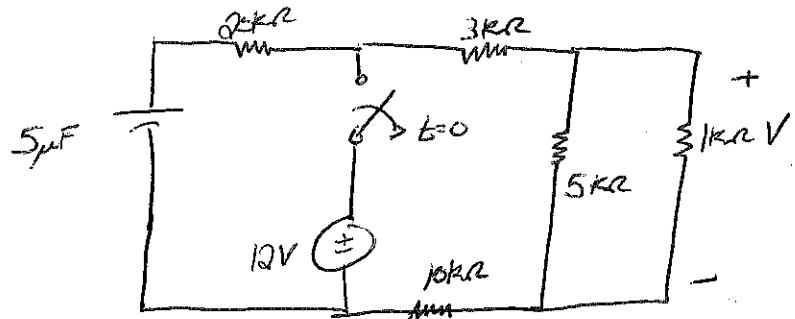


for $t < 0$

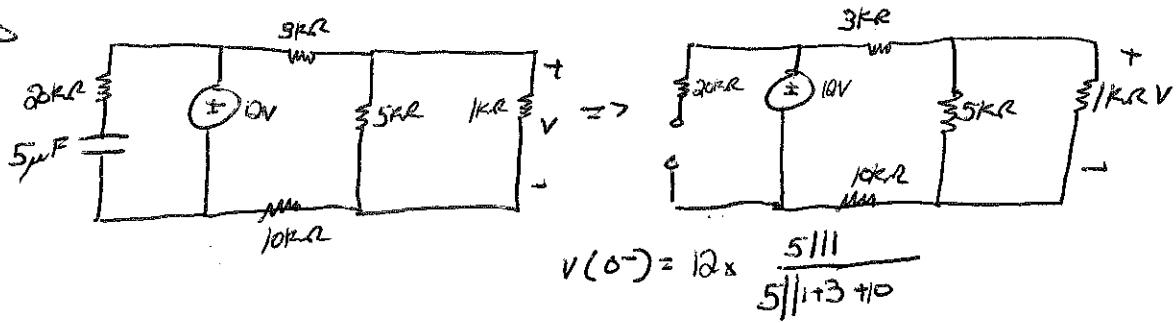

$$V_{c(0-)} = 12V = V_{c(0+)}$$

$t > 0$

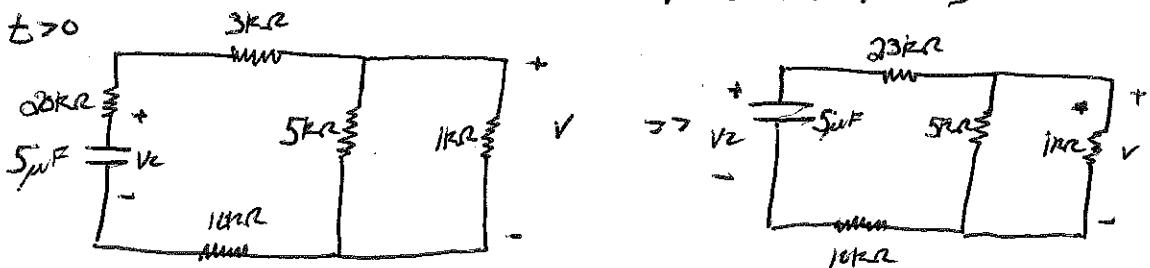

~~Req~~ $\Rightarrow R_{eq} C$

$$R_{eq} = 23k + 5k/(12+10k) = 23.833k\Omega$$



$$T = 33.833 \times 10^3 \times 5 \times 10^{-6} = 169.2 \text{ ms} \approx T$$

$$V(0^+) = 12 \times \frac{5/14}{23 + 5/(12+10)} = 12 \times \frac{5/14}{23 + 10 + 5/6} \\ = 0.2956$$

$\therefore V(t)$

$$t > 0 \Rightarrow 0.2956 e^{-\frac{t}{169.2}} V$$

Chapter 8 Exercise 27.

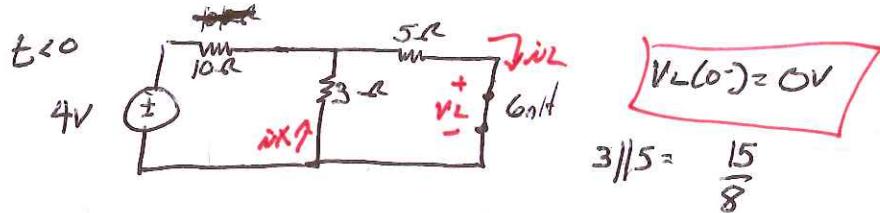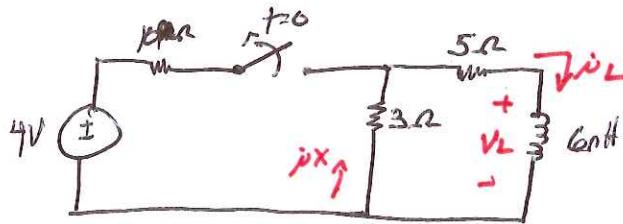

$$-j\omega X + j\omega L = \frac{4}{10 + \frac{15}{8}} = 0.3368$$

$$\Delta L = \frac{3}{8} \times 0.3368 = 0.1263 \quad \boxed{\Delta L(0+) = \Delta L(0+)} = 0.1263$$

~~$$\Delta X = 0.1263 - 0.3368 = j\Delta X(0+) = -0.2105$$~~

$$j\Delta X(0+) = j\Delta L(0+) = 0.1263 = j\Delta X(0+)$$

$$v_L(0+) = -0.1263 \times 8 = -1.0104V \quad \boxed{v_L(0+)}$$