
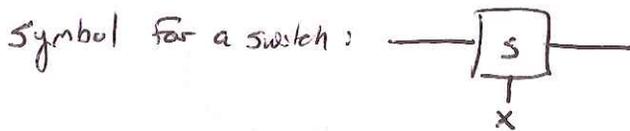


If a high voltage causes an action, then it is active-high. If a low-voltage causes an action then it is active-low.


Positive Logic: 0 is false or low state, 1 is true or high state.

Common household switches 

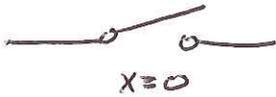Switches generally have 2 states (a binary operation). If the switch is controlled by an input x . Switch open is $x=0$, switch closed is $x=1$



light controlled switch

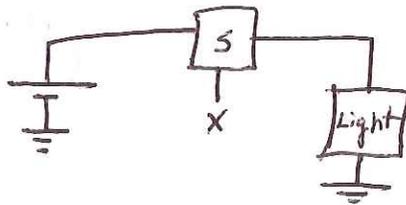

Current flows when switch is closed on $x=1$.


The output (light) is affected by the input x , if the light is on, $L=1$, if off, $L=0$. Therefore L is a function of the input x . $L=1$ if $x=1$, $L=0$ if $x=0$. Thus, $L(x)=x$ is a logical expression with an input variable

If we have two switches in series with separate inputs

$$x_1 \text{ and } x_2: L(x_1, x_2) = x_1 \cdot x_2$$


where $L=1$ if $x_1 + x_2 = 1$

$L=0$ otherwise

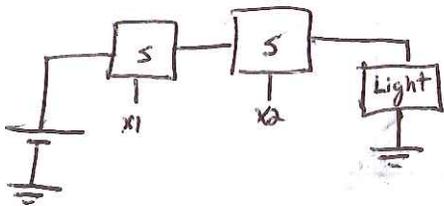

Logical AND


$$L(x_1, x_2) = x_1 \cdot x_2$$

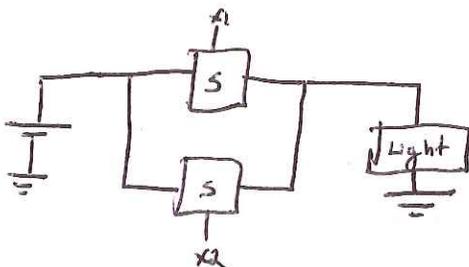

Logical OR


$$L(x_1, x_2) = x_1 + x_2$$

Series parallel connection

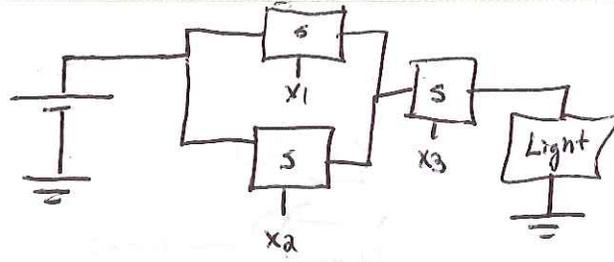

$$L(x_1, x_2, x_3) = (x_1 + x_2) \cdot x_3$$

Inverting Circuit:

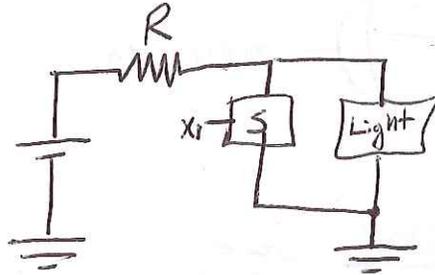

when switch is closed, current flows through short-circuit. Thus we have a NOT operation

$$L(x) = \bar{x}$$

$$L=1 : Fx=0$$

$$L=0 : Fx=1$$

Common representations of inversion/NOT

$$\bar{x} = x' = \neg x = \sim x = \text{NOT } x$$

$$f(x_1, x_2) = x_1 + x_2$$

$$\bar{f}(x_1, x_2) = \overline{x_1 + x_2}$$

Truth Tables of common logic operations

		AND	OR
x_1	x_2	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1

We can extend logic operators to more than 2 variables:

x_1	x_2	x_3	$x_1 \cdot x_2 \cdot x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

With binary and n inputs, we have 2^n possible states.


For AND operations only one instance results in 1, for OR operators, all but one instance results in 1.

Logic Gates

AND Gate



OR Gate

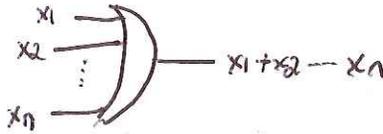

NOT Gate



NAND Gate



NOR Gate



XOR Gate

Exclusive Or



XNOR Gate

NOT Exclusive Or



XNOR Truth Table

x1	x2	Y
0	0	1
0	1	0
1	0	0
1	1	1

XOR Truth Table


$$x1 \text{ XOR } x2 = x1 \oplus x2$$

$$\star \oplus = \text{XOR} \star$$


x1	x2	Y
0	0	0
0	1	1
1	0	1
1	1	0

XOR is similar to Modulus 2

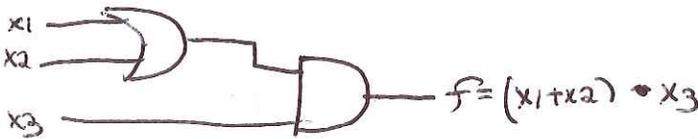Logic Gates together create networks and functions (mixed logic)



Example

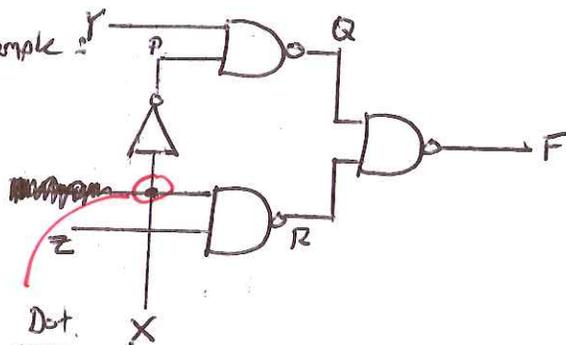

Dot means Connection

④

Inputs			Intermediate Values			Output
X	Y	Z	P = X-bar	Q = P * Y	R = X-bar * Z	F = Q * R
0	0	0	1	1	1	0
0	0	1	1	1	1	0
0	1	0	1	0	1	1
0	1	1	1	0	1	1
1	0	0	0	1	0	0
1	0	1	0	1	0	0
1	1	0	0	1	1	0
1	1	1	0	1	0	1


Gates and circuits can also compare words, but each gate and circuit does comparison on individual bits of words

word A: 11011100

word B: 01100101

$$\text{if } C = A \cdot B \rightarrow \begin{array}{r} 11011100 \\ 01100101 \\ \hline 01000100 = C = A \cdot B \end{array}$$

XOR circuit made of NAND Gates

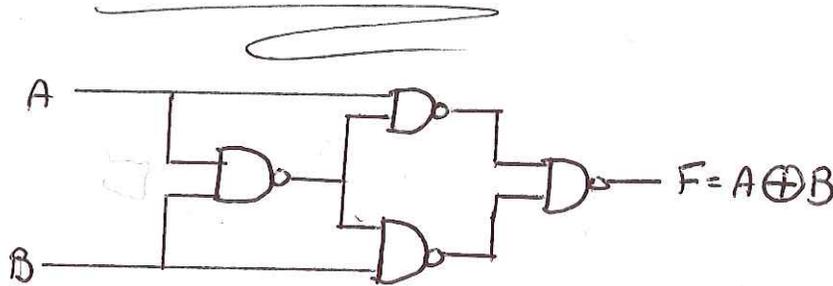

Binary Addition and Subtraction

First let's look at Binary and decimal relationship

Consider 1234 in decimal. This means we have ~~1,000~~ 1, 1000' 10^3

2, 100's 10^2

3, 10's 10^1

4, 1's 10^0

Decimal system is base 10 (0-9)

Binary is base 2 (0-1), or radix 2.

$$2^0 = 1 \quad 2^9 = 512$$

$$86_{10} = 86 \text{ base } 10 = 86 \rightarrow 8 \times 10^1 + 86 \times 10^0 = 86$$

$$2^1 = 2 \quad 2^{10} = 1024$$

$$86_{10} \text{ in base } 2 = 1 \times 2^6 + 0 \times 2^5 + 1 \times 2^4 + 0 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0$$

$$2^2 = 4 \quad 2^{11} = 2048$$

$$= 64 + 0 + 16 + 0 + 4 + 2 + 0$$

$$2^3 = 8 \quad 2^{12} = 4096$$

$$= 86_{10} = 1010110_2$$

$$2^4 = 16 \quad 2^{13} = 8192$$

$$2^5 = 32$$

$$2^6 = 64$$

$$2^7 = 128$$

$$2^8 = 256$$

Key rules for addition and subtraction:

$$1+0 = 1 \quad 1-0 = 1$$

$$1+1 = 10 \quad 10-1 = 1$$

$$1+1+1 = 11 \quad 11-1 = 10$$

$$\begin{array}{r} 101 \\ + 101 \\ \hline 1010 \end{array}$$

$$\begin{array}{r} 1011 \\ + 1011 \\ \hline 10110 \end{array}$$

$$\begin{array}{r} 111 \\ - 10 \\ \hline 101 \end{array}$$

$$\begin{array}{r} 101 \\ \times 11 \\ \hline 101 \\ 1010 \\ \hline 1111 \end{array}$$

$$\begin{array}{r} 11 \\ 11 \overline{) 1011} \\ \underline{-11} \\ 101 \\ \underline{-11} \\ 10 \end{array}$$

10 ← Remainder

Boolean Algebra + Axioms

Axioms

$$\begin{aligned} 0 \cdot 0 &= 0 \\ 1 + 1 &= 1 \\ 1 \cdot 1 &= 1 \\ 0 + 0 &= 0 \\ 0 \cdot 1 = 1 \cdot 0 &= 0 \\ 1 + 0 = 0 + 1 &= 1 \\ \text{if } x=0, \bar{x} &= 1 \\ \text{if } x=1, \bar{x} &= 0 \end{aligned}$$

Single Variable Theorems

$$\begin{aligned} x \cdot 0 &= 0 \\ x + 1 &= 1 \\ x \cdot 1 &= x \\ x + 0 &= x \\ x \cdot x &= x \\ x + x &= x \\ x \cdot \bar{x} &= 0 \\ x + \bar{x} &= 1 \\ \overline{\overline{x}} &= x \end{aligned}$$

Variable Properties

$$\begin{aligned} x \cdot y &= y \cdot x \\ x + y &= y + x \end{aligned} \left. \vphantom{\begin{aligned} x \cdot y &= y \cdot x \\ x + y &= y + x \end{aligned}} \right\} \text{commutative}$$

$$\begin{aligned} x \cdot (y \cdot z) &= (x \cdot y) \cdot z \\ x + (y + z) &= (x + y) + z \end{aligned} \left. \vphantom{\begin{aligned} x \cdot (y \cdot z) &= (x \cdot y) \cdot z \\ x + (y + z) &= (x + y) + z \end{aligned}} \right\} \text{Associative}$$

$$\begin{aligned} x \cdot (y + z) &= x \cdot y + x \cdot z \\ x + y \cdot z &= (x + z) \cdot (x + y) \end{aligned} \left. \vphantom{\begin{aligned} x \cdot (y + z) &= x \cdot y + x \cdot z \\ x + y \cdot z &= (x + z) \cdot (x + y) \end{aligned}} \right\} \text{Distributive}$$

$$\begin{aligned} x + x \cdot y &= x \\ x \cdot (x + y) &= x \end{aligned} \left. \vphantom{\begin{aligned} x + x \cdot y &= x \\ x \cdot (x + y) &= x \end{aligned}} \right\} \text{absorption}$$

$$\begin{aligned} x \cdot y + x \cdot \bar{y} &= x \\ (x + y) \cdot (x + \bar{y}) &= x \end{aligned} \left. \vphantom{\begin{aligned} x \cdot y + x \cdot \bar{y} &= x \\ (x + y) \cdot (x + \bar{y}) &= x \end{aligned}} \right\} \text{Combining}$$


$$\begin{aligned} x \cdot \bar{y} &= \overline{x + y} \\ x + \bar{y} &= \overline{x \cdot y} \end{aligned} \left. \vphantom{\begin{aligned} x \cdot \bar{y} &= \overline{x + y} \\ x + \bar{y} &= \overline{x \cdot y} \end{aligned}} \right\} \text{De Morgan's Theorem}$$

Proof of De Morgan's Law/Theorem

x	y	$x \cdot y$	$\overline{x \cdot y}$	\bar{x}	\bar{y}	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

Gate and Logic Synthesis

Some function F

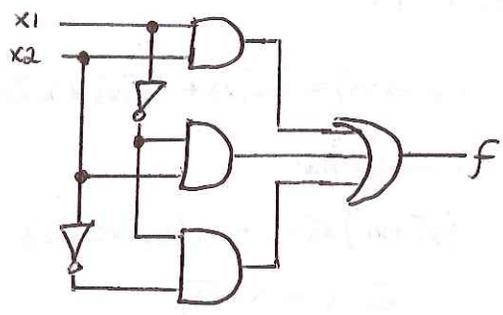

x1	x2	f(x1, x2)
0	0	1
0	1	1
1	0	0
1	1	1


$\bar{x}_1 \cdot \bar{x}_2 = f$
 $\bar{x}_1 \cdot x_2 = f$
 $\bar{x}_1 \cdot x_2 = f$
 $x_1 x_2 = f$

$f(x_1, x_2) = x_1 x_2 + \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2$
Not simplest form though!

Let's use some theorems for reduction

$f(x_1, x_2) = x_1 x_2 + \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + x_1 x_2$
 $= x_1 x_2 + \bar{x}_1 x_2 + \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2$
 $= (x_1 + \bar{x}_1) x_2 + \bar{x}_1 (\bar{x}_2 + x_2)$
 $= x_2 + \bar{x}_1$

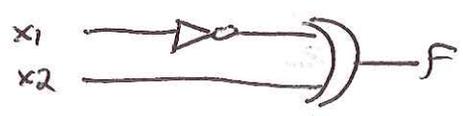$x_1 + \bar{x}_1 = 1$
 $x_2 + \bar{x}_2 = 1$



much simpler and costs less!

From truth table we can synthesize expressions for rows of $f=1$ or for rows of $f=0$.

Minterm is a sum of products
 Maxterm is a product of sums

MINTERMS + MAXTERMS

Row Number	x1	x2	x3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + \bar{x}_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + x_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + \bar{x}_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + x_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + x_3$

Row Number	x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

M SOP w/ minterms uses $f(x_1, x_2, x_3)$
with 1's

$$\therefore f(x_1, x_2, x_3) = \bar{x}_1 \bar{x}_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 \bar{x}_2 x_3 + x_1 x_2 \bar{x}_3$$

with reduction:

$$(\bar{x}_1 + x_1) \bar{x}_2 x_3 + x_1 (\bar{x}_2 + x_2) \bar{x}_3$$

$$\bar{x}_2 x_3 + x_1 \bar{x}_3$$

lower number of gates than originally thought

M POS w/ maxterms uses $f(x_1, x_2, x_3)$ with 0's

$$f(x_1, x_2, x_3) = (x_1 + x_2 + x_3)(x_1 + x_2 + \bar{x}_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3)$$

w/ commutative + associative properties

$$F = ((x_1 + x_3) + x_2)((x_1 + x_3) + \bar{x}_2)(x_1 + (\bar{x}_2 + \bar{x}_3))(x_1 + (\bar{x}_2 + \bar{x}_3))$$

$$= (x_1 + x_3)(\bar{x}_2 + \bar{x}_3)$$