
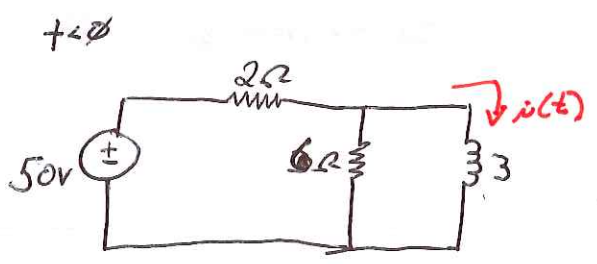



4/7/2015

Example 8.8

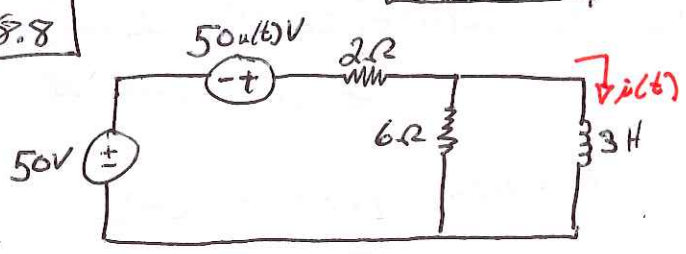


$i(t < 0) = \frac{50}{2} = 25A$

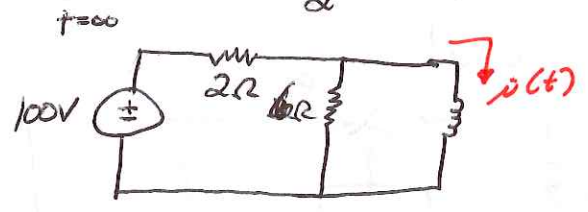when  $t \geq 0$  and  $50u(t)$  turns on, we have:



$i(t = \infty) = \frac{100}{2} = 50A$

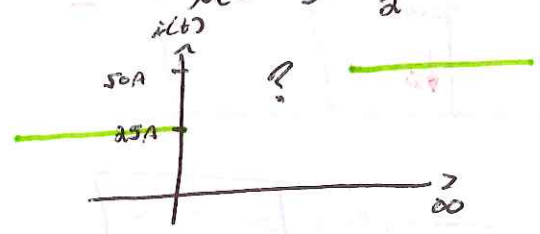

$\tau = \frac{L}{R_{eq}} = \frac{3}{3/2} = 2s \rightarrow$  settling time  $\sim 4\tau$  to  $5\tau$

$R_{eq} = \frac{2 \times 6}{2+6} = \frac{12}{8} = 1.5$

Forced response is a constant current from DC source

In general  $i = i_f + i_n$ , in our case  $i_n$  is a negative exponential

$i_n = K e^{-t/\tau} = K e^{-t/2}$

$i_f = \text{Forced} = 50A \quad \therefore i = 50 + K e^{-t/2} A \quad \text{for } t > 0$


We know prior info and fact that  $i$  can't change instantaneously

$\therefore 25 = 50 + K e^{-t/\tau} \Rightarrow 25 = 50 + K \quad \therefore K = -25$

$\therefore i = 50 - 25e^{-t/2} A \quad \text{for } t > 0$

$i = 25 A \quad t < 0$

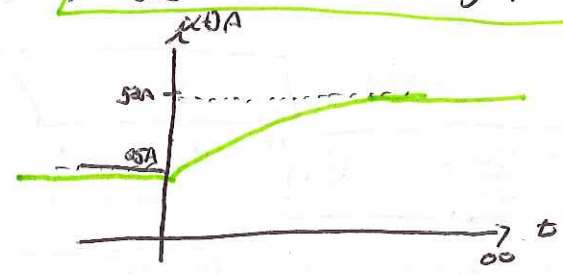using a unit step for complete response:  $i = 25 + 25(1 - e^{-t/2}) u(t) A \quad \text{for all } t$





In the most general form, remember:  $i_L = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$

$\star i_L(0^-) = i_L(0^+) \star$


$v_C = v_C(\infty) + [v_C(0^+) - v_C(\infty)]e^{-t/\tau}$

$\star v_C(0^-) = v_C(0^+) \star$

Example 8.10

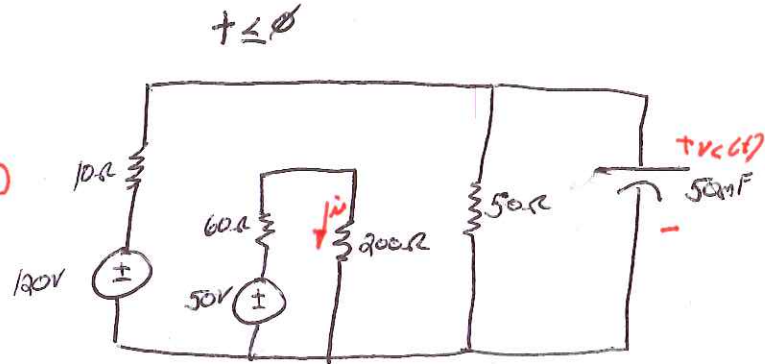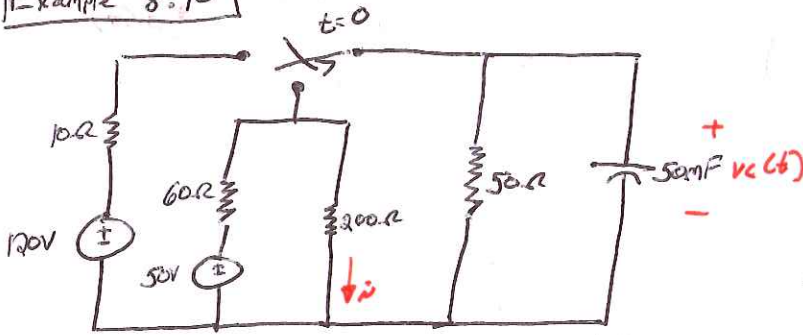

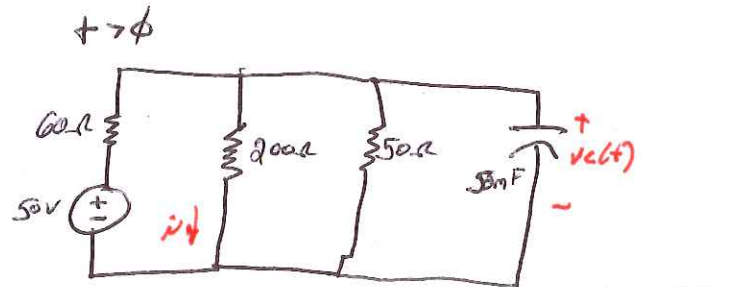$v_C(0^-) = \frac{50}{10+50} \times 120 = 100V = v_C(0^+)$



$R_{eq} = 60 \parallel 200 \parallel 50$


$40 \parallel 60 = 24\Omega = R_{eq}$

$\tau = R_{eq}C = 24 \times 50 \times 10^{-3} = 1.2$

$v_C(\infty) = \frac{40}{100} \times 50 = 20V = v_C(\infty)$  (Note:  $200 \parallel 50 = 40\Omega$ )

$\therefore v_C(t) = v_C(\infty) + [v_C(0^+) - v_C(\infty)]e^{-t/\tau} = 20 + [100 - 20]e^{-t/1.2} V \quad t \geq 0$

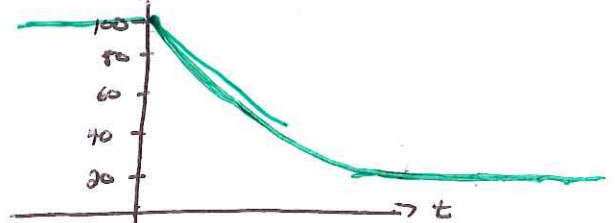$\therefore v_C(t) = 20 + 80e^{-t/1.2} u(t) V$



$i_F = \frac{20V}{200\Omega} = 0.1A = i_F = i(\infty)$

$i_N = Ae^{-t/1.2}$


$i = 0.1 + Ae^{-t/1.2}$

$i(0^+) = \frac{100}{200} = 0.5A$

$0.5 = 0.1 + A$

$\therefore A = 0.4A$

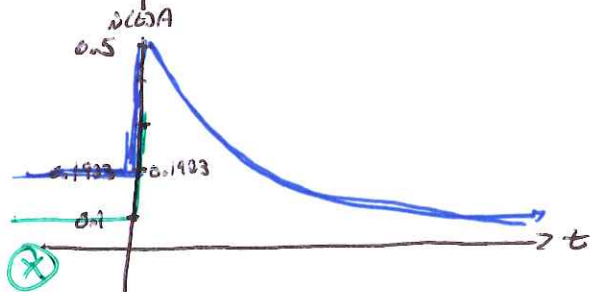also  $i(0^-) = \frac{50V}{200+100} = 0.1423A = i(0^-)$



$i(t) = 0.1423u(-t) + [0.1 + 0.4e^{-t/1.2}]u(t)$   
 $= 0.1423u(-t) + \{0.1 + [0.5 - 0.1]e^{-t/1.2}\}u(t)$


**Chapter 10**

Sinusoids + Steady state analysis.

Sinusoidally varying voltage:  $v(t) = V_m \sin \omega t$

$V_m$  = Amplitude  
 $\omega t$  = argument w/  $t$  = time +  
 $\omega$  = radians or argument Frequency

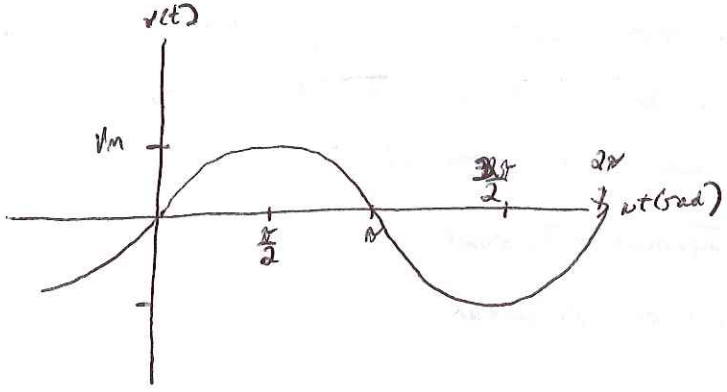
Can be plotted as a function of  $\omega t$  or  $t$



Function repeats every  $2\pi$  radians w/ period  $2\pi$  radians!

when plotted as a function of  $t$ , periods  $T$ , such that a sine wave of period  $T$ , repeats  $\frac{1}{T}$  periods per second which is its frequency  $\frac{1}{T}$  Hertz  
 $f = \frac{1}{T}$ ,  $\therefore \omega T = 2\pi$   
 such that  $\omega = \frac{2\pi}{T}$  or  $= 2\pi f$

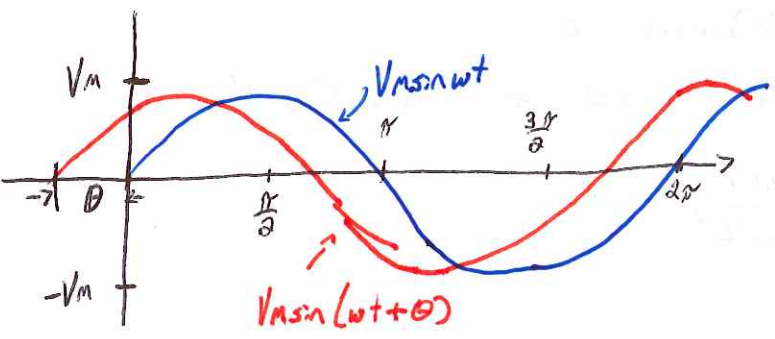More general form with phase  $\theta$   $v(t) = V_m \sin(\omega t + \theta)$



$\theta$  represents that radians the original sine wave is shifted left or right in time.

~~function~~  $V_m \sin(\omega t + \theta)$  occurs  $\theta$  radians or  $\theta/\omega$  seconds earlier than  $V_m \sin \omega t$  therefore it leads by  $\theta$

$\sin \omega t$  lags  $\sin(\omega t + \theta)$  by  $\theta$  rad or leads by  $-\theta$  rad

Phase is usually represented in degrees rather than radians

$$v = 100 \sin(2\pi 1000t - \frac{\pi}{6}) \Rightarrow v = 100 \sin(2\pi 1000t - 30^\circ)$$

- $\frac{\pi}{6} = 30^\circ$
- $\frac{\pi}{4} = 45^\circ$
- $\frac{\pi}{3} = 60^\circ$
- $\frac{\pi}{2} = 90^\circ$

sines and cosines are  $90^\circ$  out of phase

$$\sin \omega t = \cos(\omega t - 90^\circ)$$

cosine leads sine


Rules for comparing sine waves:

1. Both functions written as sines or cosines
2. Both written with positive amplitudes
3. Each have the same frequency


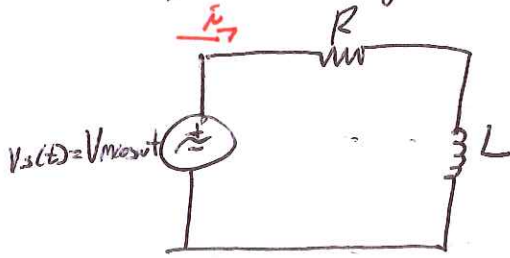
# Steady State Responses

w/ DC Forcing Functions, remain same w/ time, but what about sinusoidal sources?



$$V_m \cos \omega t = L \frac{di}{dt} + Ri$$

If at any time the derivative is  $\phi$ ,

we have  $i$  of the form  $\cos \omega t$

But when current = 0, we have the derivative proportional to  $\cos \omega t$ ,  
implying a current of  $\sin \omega t$   $\therefore$  the forced

Function may look like:  $i(t) = I_1 \cos \omega t + I_2 \sin \omega t$

where  $I_1 + I_2$  are real values that depend on  $V_m, R, L, \omega$ .

Substitute form, we have  $V_m \cos \omega t = -L \omega I_2 \sin \omega t + I_1 R \cos \omega t$

$$L[-I_2 \omega \sin \omega t + I_1 R \cos \omega t] + R[I_1 \cos \omega t + I_2 \sin \omega t]$$


rearrange + regroup

$$= (-L I_2 \omega + R I_1) \sin \omega t + (L I_1 \omega + R I_2 - V_m) \cos \omega t = 0$$

set  $t=0$  to solve for  $-L I_2 \omega + R I_1 = 0$  +  $L I_1 \omega + R I_2 - V_m = 0$

$$\text{or } I_1 = \frac{R V_m}{R^2 + \omega^2 L^2} \quad I_2 = \frac{\omega L V_m}{R^2 + \omega^2 L^2}$$

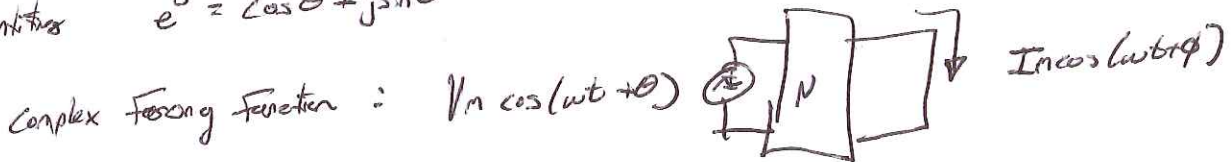Identities  $e^{j\theta} = \cos \theta + j \sin \theta$



Forcing function produces steady state current

$j = \sqrt{-1} \Rightarrow$  Imaginary Sources lead to imaginary responses



Therefore a complex source creates a complex response

$$V_m \cos(\omega t + \theta) + j V_m \sin(\omega t + \theta) \Rightarrow I_m \cos(\omega t + \phi) + j I_m \sin(\omega t + \phi)$$

$$\star \cos(\omega t + \theta) + j \sin(\omega t + \theta) = e^{j(\omega t + \theta)} \star$$

$$\therefore V_m e^{j(\omega t + \theta)} \text{ produces } I_m e^{j(\omega t + \phi)}$$

Phasors:  $e^{jx} = \cos x + j \sin x$   $3V_{dc} = ?$   $3e^{j0^\circ} = 3V$   
 Real 3, Imaginary 0

if  $v(t) = V_m \cos \omega t \rightarrow V_m \cos(\omega t + 0^\circ) \rightarrow V_m \angle 0^\circ$  polar complex form

Same notation for current

if  $i(t) = I_m \cos(\omega t + \phi)$ ,  $i(t) = \text{Re} \{ I_m e^{j(\omega t + \phi)} \}$

$$\mathbf{I} = I_m e^{j\phi}$$


In polar form  $\mathbf{I} = I_m \angle \phi$

Phasor transformer:  $i(t) = I_m \cos(\omega t + \phi) \rightarrow i(t) = \text{Re} \{ I_m e^{j(\omega t + \phi)} \}$

$$\mathbf{I} = I_m e^{j\phi} \rightarrow \mathbf{I} = I_m \angle \phi \quad \text{We know.}$$

Example 10.3

Resistor

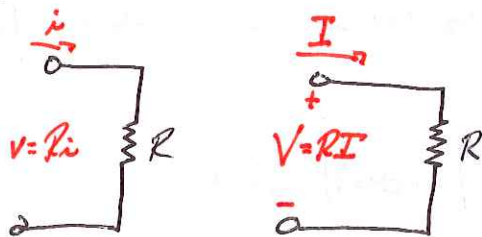

$$v(t) = Ri(t)$$

if  $v(t) = V_m e^{j(\omega t + \theta)} = V_m \cos(\omega t + \theta) + j V_m \sin(\omega t + \theta)$

resulting  $i(t) = I_m e^{j(\omega t + \phi)} = I_m \cos(\omega t + \phi) + j I_m \sin(\omega t + \phi)$

$$\therefore V_m e^{j(\omega t + \theta)} = Ri(t) = I_m e^{j(\omega t + \phi)}$$

~~in polar form~~ Remainder dividing by  $e^{j\omega t}$

$$V_m e^{j\theta} = R I_m e^{j\phi}$$

in polar form  $V_m \angle \theta = R I_m \angle \phi$

$$\therefore V = RI$$

if  $V = 8 \cos(100t - 50^\circ) V$  &  $R = 4 \Omega$

$$I = \frac{V(t)}{R} = 2 \cos(100t - 50^\circ) A$$

~~$i(t) = \frac{V(t)}{R}$~~   $\frac{8 \angle -50^\circ}{4} = 2 \angle -50^\circ A$

in phasor form  $\rightarrow$  much easier

Inductor  $V(t) = L \frac{di}{dt}$

$$V_m e^{j(\omega t + \theta)} = L I_m e^{j(\omega t + \phi)} \frac{d}{dt}$$



$$V_m e^{j(\omega t + \theta)} = j\omega L I_m e^{j(\omega t + \phi)}$$

divide by  $e^{j\omega t}$   $V_m e^{j\theta} = j\omega L I_m e^{j\phi}$

Phasor relationship:  $V = j\omega L I$

Review  $\curvearrowright$

Practice 8.9

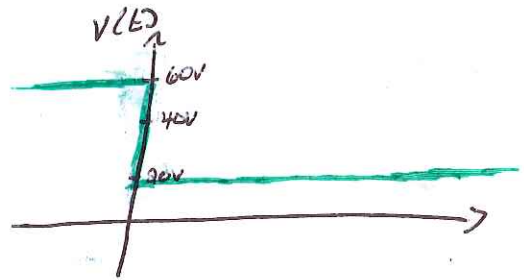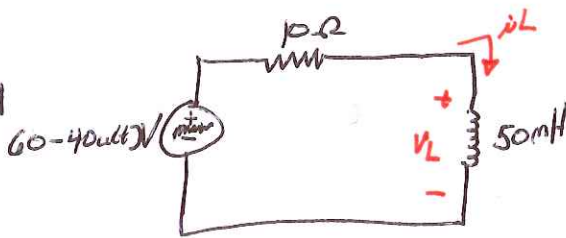

$$i_L(0^-) = \frac{60}{10} = 6A$$

$$i_L(0^+) = i_L(0^-) = 6A$$

$$i_L(\infty) = \frac{20}{10} = 2A$$

$$\tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{10} = 5 \times 10^{-4}$$

$$i_L = i_L(\infty) + [i_L(0^+) - i_L(\infty)] e^{-t/\tau}$$

$$= 2 + 4e^{-200t} \quad \text{for } t > 0$$

$$i_L(3ms) = 4.2A$$

$$v_L(0^-) = 0V$$

$$v_L(\infty) = 0V$$

$$v_L(0^+) = 20 - 10(6) = \text{voltage drop across inductor} = -40V \quad |v_L(0^+)| = 40V$$

$$v_L(3m) = 20 - 4.2 \times 10 = -21.95V \quad |v_L(3ms)| = 21.95V$$