

Homework 1

EE 2013
Fundamentals of Electric Circuits I
Prof. Rappaport

Due: September 10, 2014 @ 12:30 PM

Chapter 2 - Exercises: 8, 22, 36, 44, 45

Chapter 3 - Exercises: 2, 9, 19

Additional Problem # 1: What is the power absorbed in “?”

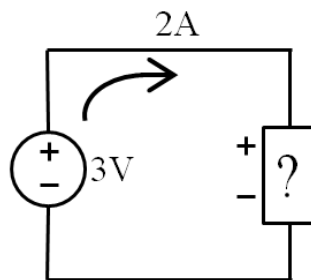


Figure 1: Extra Problem 1 Circuit

Additional Problem # 2: What is the power absorbed in “?”

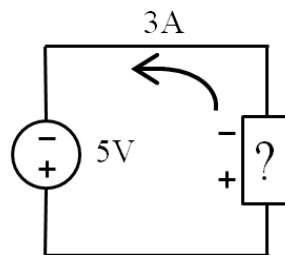


Figure 2: Extra Problem 1 Circuit