

Recitation 10 11/11/2014

Capacitors store voltage. Voltage across a capacitor cannot change instantaneously. If some DC source for a very long time, capacitor becomes open circuit & has open circuit voltage.

Current through a capacitor can change instantaneously (displacement current).


$$I = C \frac{dv}{dt} \quad \text{if voltage is constant, current flow is zero.}$$

(become current sources)
Inductors store current. Current through inductor cannot change instantaneously. If some DC current source is on for a long time, inductor becomes a short circuit current source.

Voltage across an inductor can change instantaneously. If current is constant, voltage potential is zero.

$$V = L \frac{di}{dt}$$


Simple RL circuit.

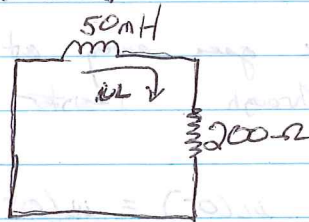

If initial current of inductor is 2A, at $t=0$

$$i_L = I_0 e^{-Rt/L}$$

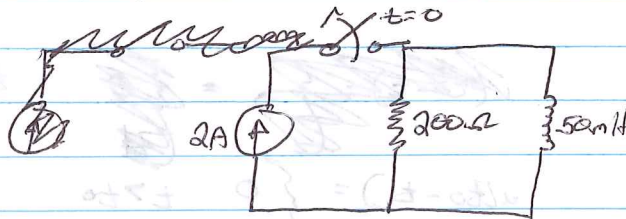
current decays over time. Think of it like this



Current source goes away at time = 0. energy leaves the circuit through dissipator in the resistor

$$\tau = \frac{L}{R}$$

Simple RC circuit

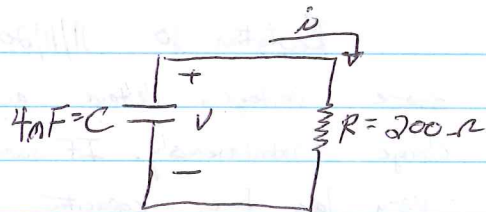

if initial voltage across capacitor = 2V at $t=0$


$$\tau = RC$$

$$V(t) = V_0 e^{-t/\tau}$$

$$V(t) = 2 e^{-t/RC}$$

Voltage potential across capacitor & decays over time
The capacitor discharges.

Think of it like this:

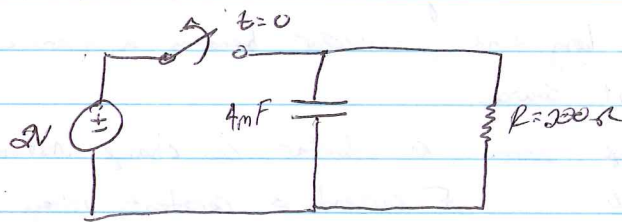


Voltage source goes away at $t=0$ energy leaves circuit through resistor after $t=0$. Voltage discharges.

For inductors $i_L(0^-) = i_L(0^+)$ after switching


For capacitors $V_C(0^-) = V_C(0^+)$ after switching

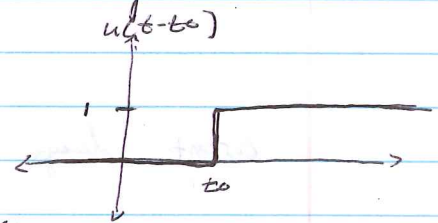
Unit step: $u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$



~~$u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$~~ = ~~$u(t-t_0) = \begin{cases} 0 & t < t_0 \\ 1 & t > t_0 \end{cases}$~~

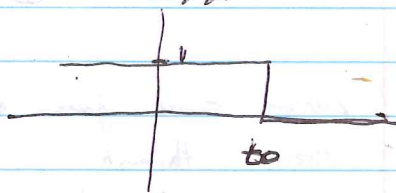~~$u(t_0-t) = \begin{cases} 0 & t > t_0 \\ 1 & t < t_0 \end{cases}$~~



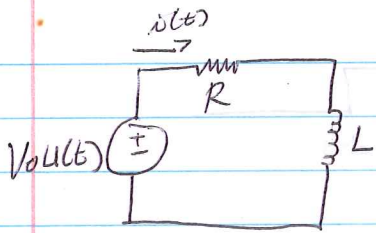

$$Ri + L \frac{di}{dt} = 0$$

$$i = 0, \frac{di}{dt} = 0$$

$$t \geq 0, Ri + L \frac{di}{dt} = V_0 u(t)$$

$$u(t) = 1 \quad t \geq 0 \quad Ri + L \frac{di}{dt} = V_0$$


$$\frac{L di}{dt} = V_0 - Ri$$

$\frac{L di}{V_0 - Ri} = dt$ if you solve and reduce, you get

$$i = \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-Rt/L} \right) u(t)$$

Think about it: Inductor starts to store current.

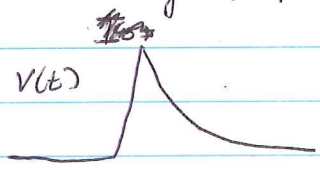Initially sharp voltage jump, then decay.





Inverse of each other

$$V_L(t) = V_0 e^{-Rt/L}$$

$$\text{initially } i(t) = \left(\frac{V_0}{R} - \frac{V_0}{R} e^{-Rt/L} \right) u(t)$$

settles towards current
Steady state short circuit current
goes to 0 at ∞


Example 8.8

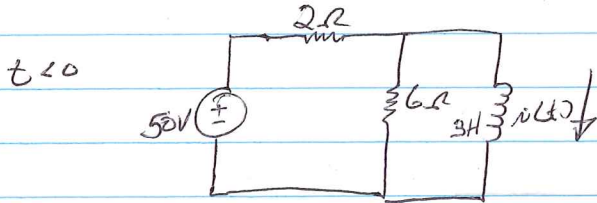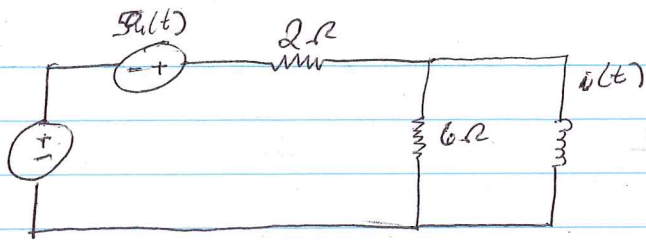

$$i(t) = 50 \text{ A current} = \frac{50}{2} = 25 \text{ A}$$

when $50u(t)$ turns on, $i(t)$ changes to ~~25~~ $\frac{100}{2} = 50 \text{ A}$.

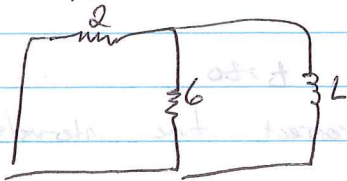~~...~~ $\tau \rightarrow$ open inductors




$$L = 3 \text{ H}$$

$$R_{eq} = 2 \parallel 6 = \frac{12}{8} = \frac{3}{2}$$



$$\tau = \frac{L}{R} = \frac{3}{3/2} = 2$$

~~...~~ $i(t) = \frac{50}{2} + \frac{50}{2} (1 - e^{-t/\tau})$

$$= 25 + 25(1 - e^{-t/2}) u(t)$$

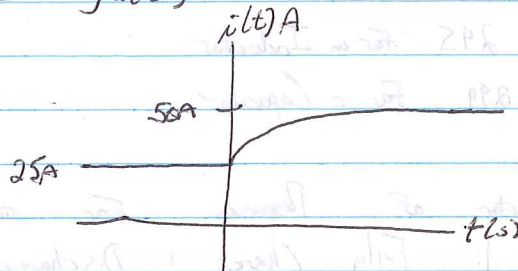

Example 8.9

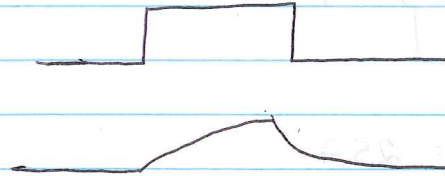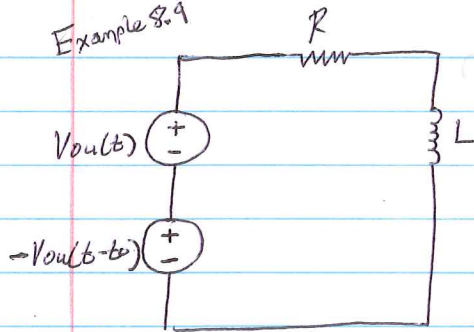

$$i_1(t) \text{ when pulse is on} = \frac{V_0}{R} (1 - e^{-R(t-t_0)/L})$$

$$= \frac{V_0}{R} - \frac{V_0}{R} e^{-Rt/L} \quad t > 0 \quad i_1 = 0 \text{ at } t = 0$$

other source: $= -\frac{V_0}{R} (1 - e^{-R(t-t_0)/L}) \quad t > t_0$


can add solutions together over correct time intervals

$$i(t) = \begin{cases} \frac{V_0}{R} (1 - e^{-Rt/L}) & 0 < t < t_0 \\ \frac{V_0}{R} (1 - e^{-Rt/L}) - \frac{V_0}{R} (1 - e^{-R(t-t_0)/L}) & t > t_0 \end{cases}$$

~~Page~~
 Page 295 For an Inductor
 Page 299 For a Capacitor

Predictor of Responses For switching circuits Page 301

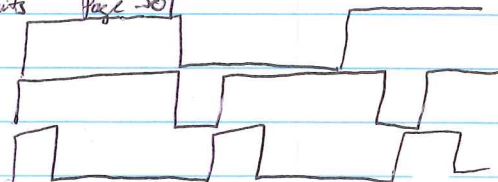- Case 1: Fully charge & Discharge
- Case 2: Fully charge but not fully discharge
- Case 3: no time to fully charge, but to discharge
- Case 4: no time to fully charge or charge



Find R_{TH}

<4> Source Transformation




<1> finding V_{oc} & I_{sc} , take their ratio


<2> Setting all independent source to zero, and using resistor combination technique

<3> Connecting an unknown ^{test} current source to the terminal, Zero out all other source, finding an algebraic expression for voltage/current, taking the ratio.

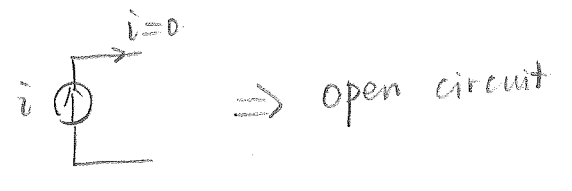Q: How to zero out or set a source to zero?



eg. HW 7. Chapter 5. 35.

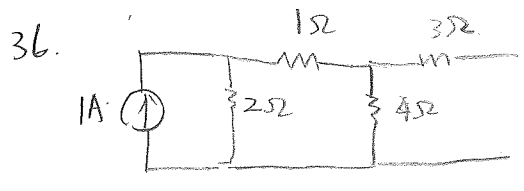

find R_{TH} .

* When we do superposition. \rightarrow zero out.

open current source.

short voltage source.

* Time Constant (unit: s).

$$\tau = \frac{L_{eq}}{R_{eq}}$$

$$\tau = RC_{eq}$$


How to find L_{eq} , R_{eq} , C_{eq}

Ex 8.4 (textbook)


Thevenin equivalent resistance seen by energy storage element (zero out independent sources)

<1> R_{TH} is the equivalent resistance "seen" by the inductor

Basic Circuit

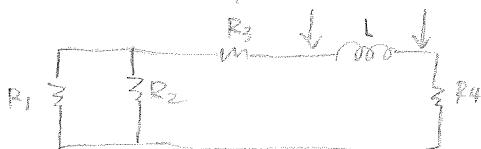


$$R_{eq} = R_3 + R_1 // R_2 + R_4$$

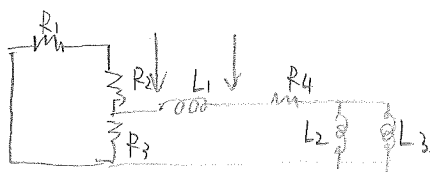


$$R_{eq} = (R_1 + R_2) // R_3 + R_4$$

$$L_{eq} = L_1 + L_2 // L_3$$

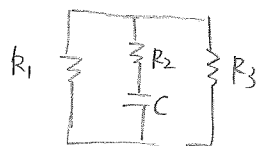

$$R_{eq} = R_2 + R_1 // R_3$$


$$\frac{48}{0.8} = 60$$

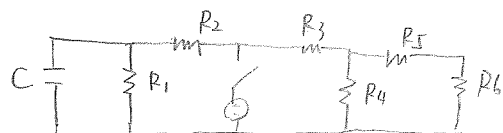

$$R_{eq} = \left\{ \left[(R_5 + R_6) // R_4 \right] + R_2 + R_3 \right\} // R_1$$

<2> Complicated Circuit (with dependent source) Thevenin:

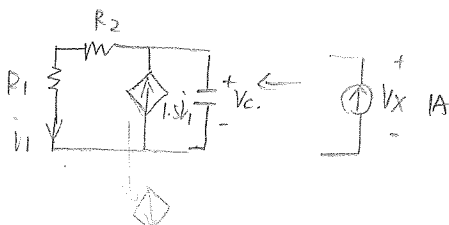Connecting a test source to determine the equivalent



$$V_x = (1.5i_1 + i_1)(R_1 + R_2)$$

$$\leftarrow R_1 = 20 \Omega$$

$$R_2 = 10 \Omega$$

$$i_1 = \frac{V_x}{R_1 + R_2}$$

$$V_x = -60V$$

$$R_{eq} = -60 \Omega$$

$$\tau = -60 \mu s$$

↑
exponentially increase

