
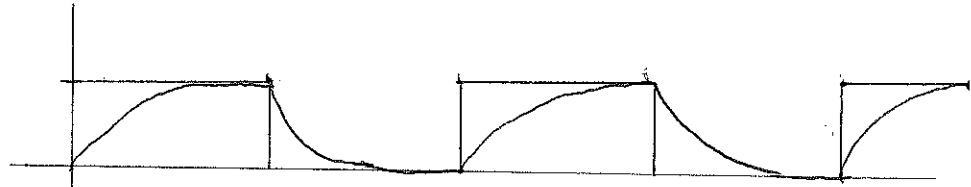


Page 302-304, Charging + Discharging properties of Capacitors + Inductors.


Case I: Fully Charge + Discharge

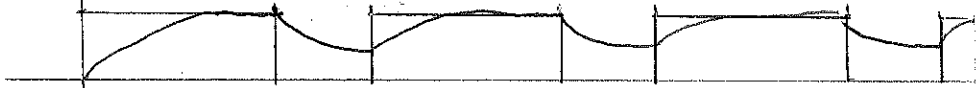


Case II: Fully Charge but not Discharge



Case III: Fully Discharge, not charge

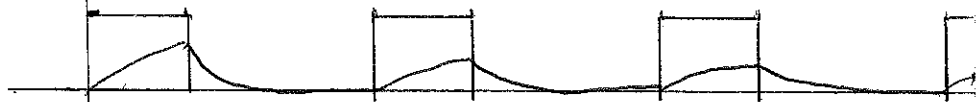

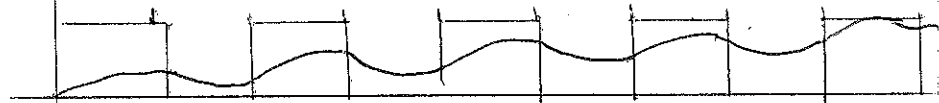Case IV: No time to fully charge or discharge



Two solutions to Differential equation for RLC circuits

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

general solution for voltage:  $v = A_1 e^{s_1 t}$

Substitute  $v_1 = A_1 e^{s_1 t}$   
 $v_2 = A_2 e^{s_2 t}$

Linearity proves ~~that~~ sum of 2 solutions is a solution:  $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

For  $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$s_1 + s_2$  are dimensionless here  
units defined per-second.

$\frac{1}{2RC} + \frac{1}{\sqrt{LC}}$  also have  $s^{-1}$  units.  $\frac{1}{s} = \text{Hz}$  is Frequency.

$\omega_0 = \text{Fundamental or resonant Frequency} = \frac{1}{\sqrt{LC}}$

$\frac{1}{2RC}$  is the neper Frequency, or exponential damping factor,  $\alpha = \frac{1}{2RC}$

Rate at which natural response decays or damps to steady state.

$s_1, s_2$  are complex frequency.

So, for  $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$

$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$

$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$

$\alpha = \frac{1}{2RC}$

$\omega_0 = \frac{1}{\sqrt{LC}}$

$A_1 + A_2$  are found by solving initial conditions

Relationship	s values	Descriptor
$\alpha > \omega_0$	$s_1 + s_2$ are real	overdamped
$\alpha < \omega_0$	$s_1 + s_2$ are complex	underdamped
$\alpha = \omega_0$	real value, just $\alpha$	critically damped.

Example 9.1  $L = 10 \text{ mH}$ ,  $C = 100 \mu\text{F}$

Find R ranges for over + under damped.

$\omega_0 = \frac{1}{\sqrt{LC}}$

$\alpha = \frac{1}{2RC}$

Overdamped:  $\frac{1}{2RC} > \frac{1}{\sqrt{LC}} \rightarrow \frac{\sqrt{LC}}{2RC} > R \cdot \frac{(10 \times 10^{-3})(10 \times 10^{-6})}{2(10 \times 10^{-6})} > R \quad R < 5$

② Underdamped  $R > 5$

Over-damped RLC circuit  $v(t) \rightarrow A_1 e^{s_1 t} \rightarrow 0$  as  $t \rightarrow \infty$

$$v(0) = A_1 e^{s_1 \cdot 0} + A_2 e^{s_2 \cdot 0} = A_1 + A_2 = v(0)$$

then use initial conditions on capacitor

$$i_C = C \frac{dv}{dt}$$

$$\frac{dv}{dt} = s_1 A_1 e^{s_1 t} + s_2 A_2 e^{s_2 t}$$

evaluate at  $t=0$   $\frac{dv}{dt} \Big|_{t=0} \rightarrow s_1 A_1 + s_2 A_2$

$$\frac{dv}{dt} \Big|_{t=0} = \frac{v(0)}{C}$$



use this and

to solve for  $A_1 + A_2$

Use table ~~on page~~ 9.1

on page 347 Response equations are given

Practice 9.2

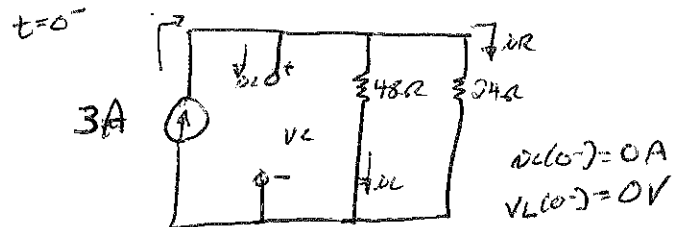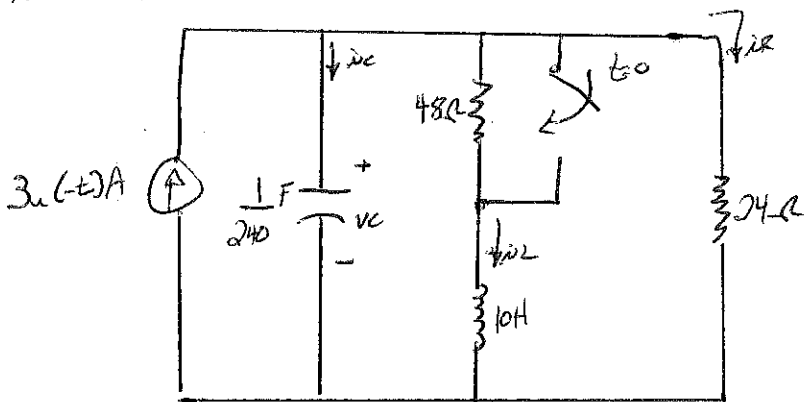

$$a) i_L(t=0^-) = \frac{3 \times 24}{24+48} = 1A$$


$$b) v_C(t=0^-) = 3 \times (48 \parallel 24) = 3 \times \frac{48 \times 24}{48+24} = 48V$$

$$i_L(t=0^-) = i_L(t=0^+) = 1A$$

$$c) i_R(t=0^+) = 3 - i_L(t=0^+) = 3 - 1 = 2A = i_R(t=0^+)$$

$$d) i_C(t=0^+) = -i_L(t=0^+) - i_R(t=0^+) = -3A$$

$$e) v_C(t=0^+)$$

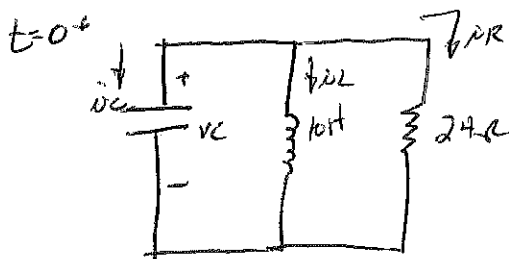

$$\alpha = \frac{1}{2RC} = 5s^{-1}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 4854 \text{ rad/sec}$$

$\alpha > \omega_0 \rightarrow$  overdamped.

$$A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$v_C(t) = C \frac{dv_C}{dt} = C [A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}]$$

$$\text{use } v_C(t=0^+) = A_1 + A_2 = 48V$$

solve rest

