

Restatan 12 - 11/25/2014

Complete response of RLC circuits is similar to RL + RC circuits. Forced responses are produced from DC sources that are switched on or off in the circuit, such that the response may not vanish at $t = \infty$

Steps

- ① Determine initial conditions
- ② Obtain numerical value for the forced response
- ③ Write appropriate form of the natural response with the necessary number of arbitrary constants
- ④ Add forced response + natural response to make complete response
- ⑤ Evaluate response and its derivative at $t = 0$ and employ initial conditions to solve for unknown constants

In general for voltage, forced response $v_F(t) = V_F$


natural response $v_n(t) = A e^{s_1 t} + B e^{s_2 t}$

$\therefore v(t) = V_F + A e^{s_1 t} + B e^{s_2 t}$


more difficult portion is derivative of response $\frac{dv}{dt} = 0 + s_1 A e^{s_1 t} + s_2 B e^{s_2 t}$
with $\frac{dv}{dt}$ at $t = 0^+$

Example 9.9

Circuit:

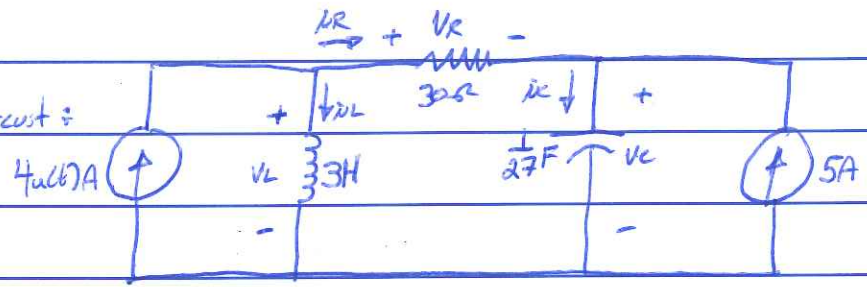

$t = 0^-$

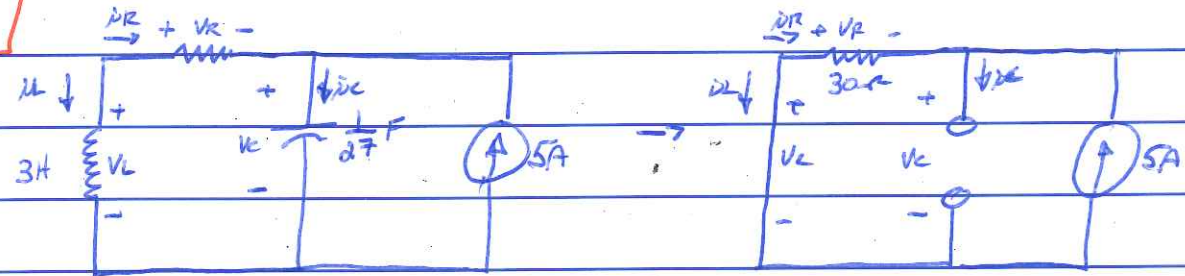


- ① $i_C(0^-) = 0 \text{ A}$
- ② $i_R(0^-) = -5 \text{ A}$
- ③ $i_L(0^-) = 5 \text{ A}$
- ④ $v_C(0^-) = 150 \text{ V} = 5 \times 30$
- ⑤ $v_R(0^-) = -150 \text{ V} = -5 \times 30$
- ⑥ $v_L(0^-) = 0 \text{ V}$

For $t = 0^+$ what cannot change?

$v_C(0^-) = v_C(0^+) = 150 \text{ V}$ (4) $i_L(0^-) = i_L(0^+) = 5 \text{ A}$ (3)

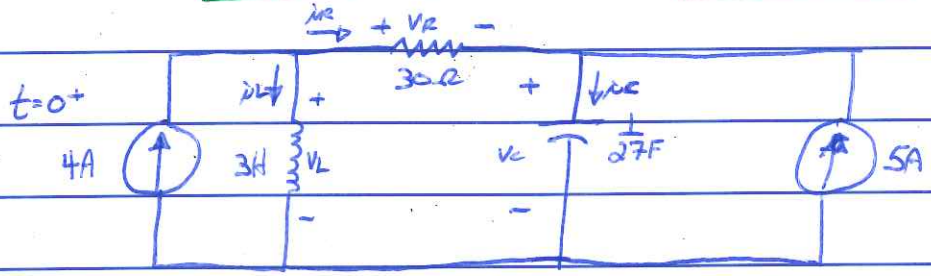$\omega_0 = \frac{1}{\sqrt{3 \times 27}} = 3 - \omega_0$
 $\alpha = \frac{1}{2 \times 27} = \frac{1}{54}$
 Series: $\frac{R}{L} = \frac{30}{6} = 5 = \alpha$ $\alpha > \omega_0$



$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$
 $s_1 = -1$ $s_2 = -2$

- i_L can't change instantaneously, so $i_R(0^+) = i_R(0^-) + 4 \text{ A} = i_R(0^+) = -1 \text{ A}$ (2)
- $\therefore v_R(0^+) = 30 \times (-1) = -30 \text{ V}$ (5) $i_C(0^+) = i_R(0^+) + 5 = -1 + 5 = 4 \text{ A} = i_C(0^+)$ (1)
- $v_L(0^+) = v_R(0^+) + v_C(0^+) = -30 + 150 = 120 \text{ V} = v_L(0^+) = 120 \text{ V}$ (6)

Forced response of Cir is 150V, $v_C(t) = 150 + Ae^{-t} + Be^{-2t}$

$v_C(0^+) = 150 \therefore 150 = 150 + A + B \therefore A + B = 0$

$\frac{dv_C}{dt} = -Ae^{-t} - 2Be^{-2t}$

$i_C = C \frac{dv_C}{dt}$ $i_C(0^+) = 4 = C \frac{dv_C}{dt}$

$\therefore \frac{4}{C} = -Ae^{-t} - 2Be^{-2t} \Big|_{t=0} \rightarrow \frac{4}{27} = -A - 2B$

$108 = -A - 9B$ $-A = 108 + 9B \therefore B = -13.5$

$A = 13.5$

$\therefore v_C(t) = 150 + 13.5(e^{-t} - e^{-2t}) \text{ V}$


Sinusoids : sinusoidally varying voltage $v(t) = V_m \sin(\omega t)$

$V_m =$ amplitude

$\omega t =$ argument where t is time,

ω is radian or angular frequency


may be plotted as a function of t or ωt

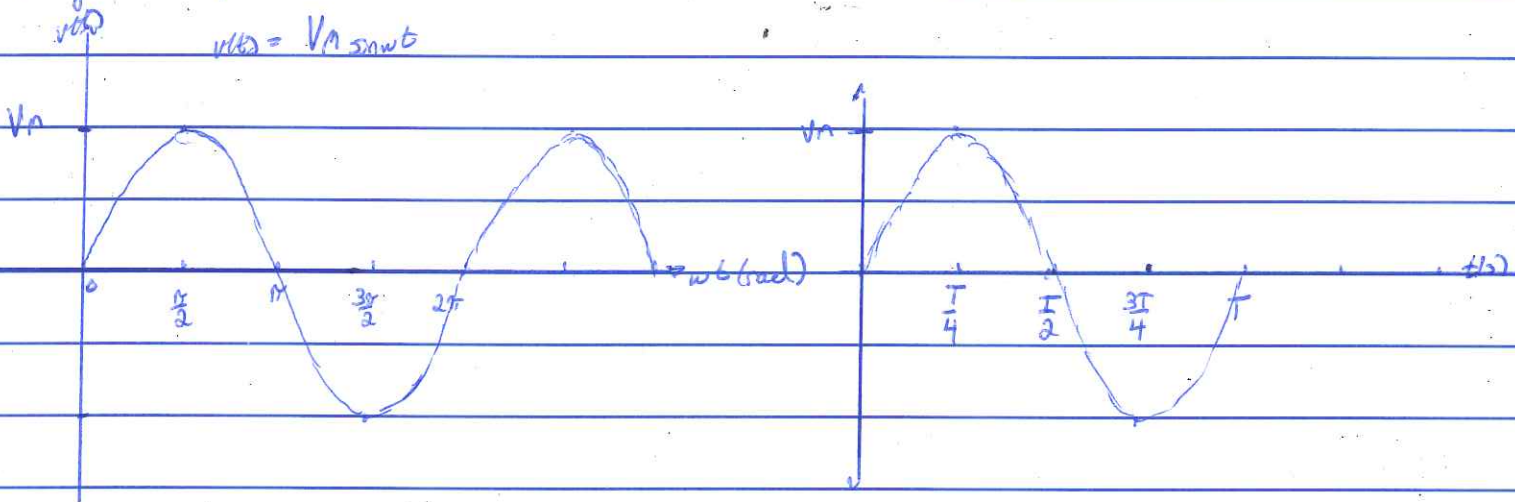

Periods 2π radians, it's periodic every 2π

as a function of t , period is T , executes every $\frac{1}{T}$ periods each second.
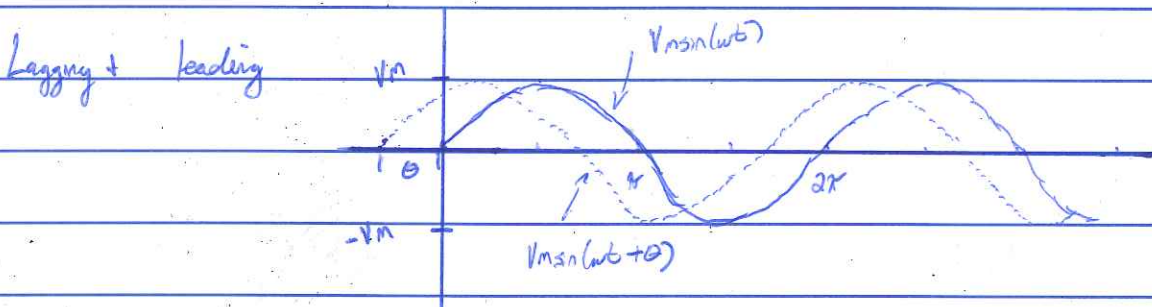
$$f = \frac{1}{T} \quad \omega T = 2\pi \quad \therefore \omega = 2\pi f$$



Sines to cosines is just 90° phase shift

Phasors : $e^{jx} = \cos x + j \sin x$

3V DC source = $3e^{j0} = 3V$

can represent everything in terms of $e^{j\omega t}$

if $v(t) = V_m \cos \omega t = V_m \cos(\omega t + 0^\circ) \rightarrow V_m \angle 0^\circ$ (polar) complex

can represent current as $i(t) = I_m \cos(\omega t + \phi) = I_m \angle \phi$ ← phasor

Steps for turning in to a phasor if $i(t) = I_m \cos(\omega t + \phi)$, it is expressed as the real part of Euler's identity $\rightarrow i(t) = \text{Re} \{ I_m e^{j(\omega t + \phi)} \}$

can drop $e^{j\omega t}$ + simply represent $I = I_m e^{j\phi}$, in polar $I_m \angle \phi = I$



Process ① $i(t) = I_m \cos(\omega t + \phi)$

② $i(t) = \text{Re} \{ I_m e^{j(\omega t + \phi)} \}$

③ $I = I_m e^{j\phi}$

④ $I = I_m \angle \phi \rightarrow$ frequency domain representation

magnitude change over phasor angle

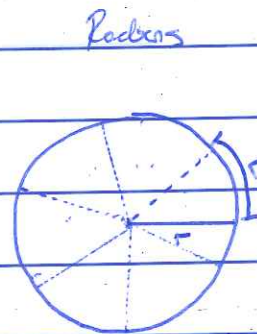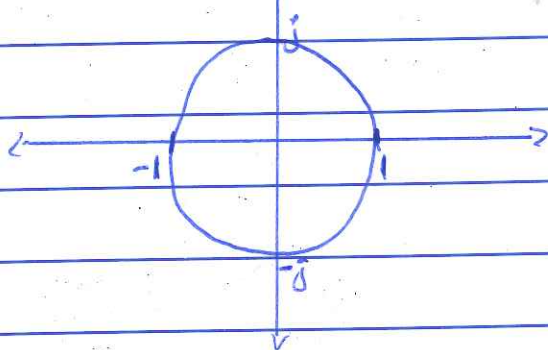

circumference is

2π radians

We can represent everything as phasors!

~~v(t) = R i(t)~~

Appendix 5 Complex #'s

Page 817

General Expressions $e^{j\theta} = \cos\theta + j\sin\theta$
 $e^{-j\theta} = \cos\theta - j\sin\theta$

in general $V_m(\cos\omega t + j\sin\omega t) \rightarrow V_m e^{j\omega t}$


$v(t) = R i(t) \rightarrow v(t) = V_m e^{j(\omega t + \phi)} = V_m \cos(\omega t + \phi) + j V_m \sin(\omega t + \phi)$

$i(t) = I_m e^{j(\omega t + \phi)} = I_m \cos(\omega t + \phi) + j I_m \sin(\omega t + \phi)$

$\therefore V_m e^{j(\omega t + \phi)} = R i(t) = R I_m e^{j(\omega t + \phi)}$

$V_m e^{j\phi} = R I_m e^{j\phi}$

$V_m \angle \phi = R I_m \angle \phi$

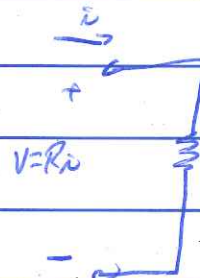

Inductor $v(t) = L \frac{di}{dt}$ in phasor form \rightarrow

① $V_m e^{j(\omega t + \phi)} = L \frac{d}{dt} I_m e^{j(\omega t + \phi)}$

② $V_m e^{j(\omega t + \phi)} = j\omega L I_m e^{j(\omega t + \phi)}$

③ $V_m e^{j\phi} = j\omega L I_m e^{j\phi} \quad \therefore \boxed{V = j\omega L I}$

Capacitor $i(t) = C \frac{dv(t)}{dt}$

$$\textcircled{1} \quad \cancel{I_{me}} \quad I_{me}^{j(\omega t + \phi)} = C \frac{d}{dt} V_{me}^{j(\omega t + \phi)}$$

$$\textcircled{2} \quad I_{me}^{j(\omega t + \phi)} = j\omega C V_{me}^{j(\omega t + \phi)}$$

$$\textcircled{3} \quad I_{me}^{j\phi} = j\omega C V_{me}^{j\phi}$$

$$\textcircled{4} \quad \therefore I = j\omega C V$$

In general For $R \rightarrow V = RI$

$L \rightarrow V = j\omega L I$

$C \rightarrow V = \frac{1}{j\omega C} I$