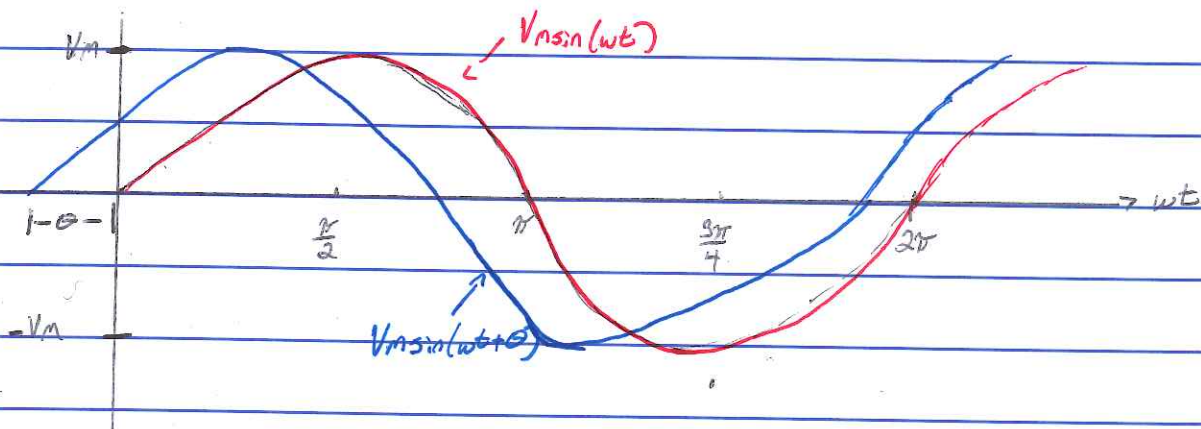


Precitation 13 - 12/2/2014



we can say that $V_m \sin(\omega t)$ lags $V_m \sin(\omega t + \theta)$ by θ radians
 or that $V_m \sin(\omega t)$ leads $V_m \sin(\omega t + \theta)$ by $-\theta$ radians

These sinusoids are out of phase, but sinusoids with the same phase are in phase with each other

Sines and Cosines are out of phase by 90°

In general $\sin \omega t = \cos(\omega t - 90^\circ)$

or $\sin(\omega t + 90^\circ) = \cos(\omega t)$

In this case the sine leads the cosine

Practice 10.1 $v_1 = 120 \cos(120\pi t - 40^\circ) V$

a) $i_1 = 2.5 \cos(120\pi t + 20^\circ) A$ i_1 lags by $-40 - 20 = -60^\circ$


b) $i_2 = 1.4 \sin(120\pi t - 70^\circ) A = 1.4 \cos(120\pi t - 160^\circ)$; i_2 lags by $-40 - 160 = 120^\circ$

c) $i_3 = -0.8 \cos(120\pi t - 110^\circ) A \Rightarrow$ ~~lags by~~ $\rightarrow 0.8 \cos(120\pi t + 70^\circ)$ i_3 lags by $-40 - 70 = 70^\circ$

Identities $e^{j\theta} = \cos \theta + j \sin \theta$

$V_m \cos(\omega t + \theta - 90^\circ) = V_m \sin(\omega t + \theta)$


In general

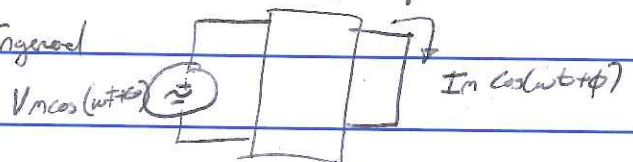

Imaginary Sources lead to imaginary responses!

Imaginary Source $\rightarrow V_m \cos(\omega t + \theta) + j V_m \sin(\omega t + \theta) \rightarrow V_m e^{j(\omega t + \theta)}$

Example 10.2

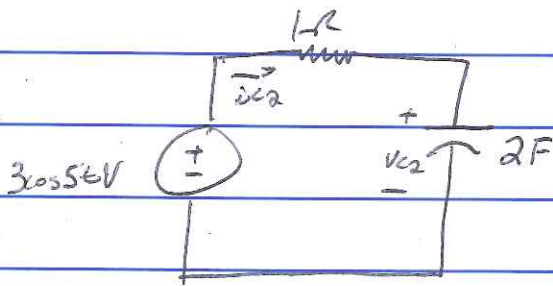

$$i = C \frac{dv}{dt}$$

By Definition $V_s = v_{c2} \times 1 + v_{c2} = 0$

$$v_{c2} = \frac{C dv_{c2}}{dt}$$

$$\therefore 3e^{j5t} = 2 \times \frac{dv_{c2}}{dt} + v_{c2}$$

$$\therefore -3e^{j5t} + 2 \frac{dv_{c2}}{dt} + v_{c2} = 0$$

at steady steady $v_{c2} = V_m e^{j5t}$ in general form

$$\therefore -3e^{j5t} + 2 \times V_m e^{j5t} \frac{d}{dt} + V_m e^{j5t} = 0$$

$$-3e^{j5t} + 10j V_m e^{j5t} + V_m e^{j5t} = 0$$

$$V_m e^{j5t} (10j + 1) = 3e^{j5t}$$

$$V_m = \frac{3}{(10j+1)} \quad || = \frac{3}{\sqrt{10^2+1^2}} \quad \angle -\tan^{-1}(10/1) V$$

$$\therefore V_m = \frac{3}{\sqrt{101}} \quad \angle -\tan^{-1}(10/1) V$$

where $\text{Re}\{v_{c2}\} = \text{Re}\{V_m e^{j5t}\} \rightarrow \text{Re}\left\{\frac{3}{\sqrt{101}} \angle -\tan^{-1}(10/1) e^{j5t}\right\}$

$$= 0.2985 \cos(5t - 84.3^\circ) V = v_{c2}$$

Phasor Form

IF $v(t) = V_m \cos(\omega t)$, $V = V_m \angle 0 = V_m \angle 0$

IF $i(t) = I_m \cos(\omega t + \phi)$, $I = I_m \angle \phi$

Appendix 5 helps w/ complex #'s
+ Euler's identity

Still holds true that $V = RI$

$$v(t) = 100 \cos(400t - 30^\circ) \text{ V}$$

$$V = 100 \angle -30^\circ \text{ V}$$

Inductor $L \rightarrow V = j\omega L I$

From $V = \frac{L di}{dt}$

Capacitor $C \rightarrow I = j\omega C V$

From $I = C \frac{dv}{dt}$

Φ From $V \rightarrow V_m e^{j(\omega t + \theta)}$

$I \rightarrow I_m e^{j(\omega t + \phi)}$

$$V_m e^{j(\omega t + \theta)} = L \frac{I_m e^{j(\omega t + \phi)}}{dt}$$

$$= V_m e^{j\omega t + j\theta} = L j\omega I_m e^{j\omega t + j\phi} \rightarrow V_m e^{j\theta} = L j\omega I_m e^{j\phi} \therefore \underline{V = L j\omega I}$$

Example 10.4

Apply $8\angle -50^\circ \text{ V}$ at a frequency of $\omega = 100 \text{ rad/s}$ to a 4 H inductor
determine phasor current + time-domain.

By Definition $I = \frac{V}{j\omega L}$

$$\frac{8\angle -50^\circ \text{ V}}{j(100)(4)} = \frac{8\angle -50^\circ}{400 \angle 90^\circ} \rightarrow \frac{8}{400} \angle -140^\circ$$

$$\therefore I = 0.02 \angle -140^\circ \text{ A}$$

Impedance + Admittance $\frac{V}{I} = R$

$j \frac{V}{I} = j\omega L$

$j \frac{V}{I} = \frac{1}{j\omega C}$

Admittance is opposite of reactance.