

□ = element  
 7 elements  
○ = node  
 4 nodes  
| = branch  
 6 branches

node: a point at which 2 or more elements share a common connection  
 a wire can be a node.

branch: a single path in a network where one simple element has  
 a node at each end.

Chapter 2: centi:  $10^{-2}$

milli:  $10^{-3}$

micro:  $10^{-6}$

nano:  $10^{-9}$

pico:  $10^{-12}$

femto:  $10^{-15}$

kilo:  $10^3$

mega:  $10^6$

giga:  $10^9$

tera:  $10^{12}$

peta:  $10^{15}$

electron =  $-1.602 \times 10^{-19} \text{ C}$

proton =  $+1.602 \times 10^{-19} \text{ C}$

current is rate of charge flow  $i = \frac{dq}{dt}$

Derivative:  $2x \frac{d}{dx} = 2 = \text{rate of change} = \text{slope}$


charge transferred between  $t_0$  to  $t$  is  $\int_{q(t_0)}^{q(t)} dq = \int_{t_0}^t i dt'$

$\therefore$  total charge transferred over time:  $q(t) = \int_{t_0}^t i dt' + q(t_0)$   
C/s

Voltage: potential difference between 2 points. "voltage across element"


1 Volt = 1 J/C

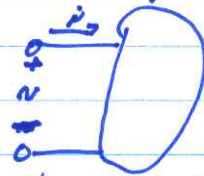Power =  $VI = \frac{\text{J}}{\text{C}} \times \frac{\text{C}}{\text{s}} = \text{J/s}$




element absorbs  $V \cdot I$  power


supplies  $-V \cdot I$  power

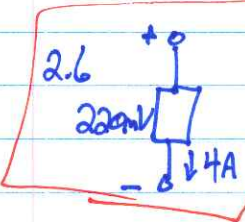

Power absorbed? 880 mW

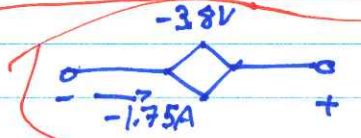

Power generated?

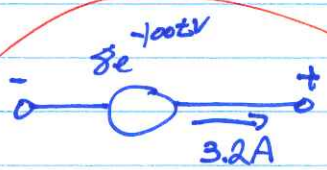


Power absorbed =  $1.75 \text{ A} \times 38 \text{ V}$   
=  $-6.65 \text{ W absorbed}$   
=  $6.65 \text{ W generated}$


Power Delivered to circuit?  
 $t_1 = t_2 = 5 \text{ ms}$

$$-3.2 \text{ A} \times 8e^{-100(5 \times 10^{-3})} = -15.53 \text{ W}$$

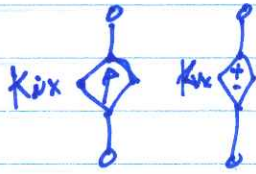Independent sources. Voltage is always the same regardless of current flowing



K is a dimensionless scaling constant.

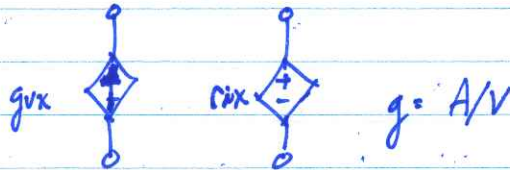


$$g = A/V$$

Scaling factors where  $V_x$  &  $I_x$

are defined in the circuit.

2.9

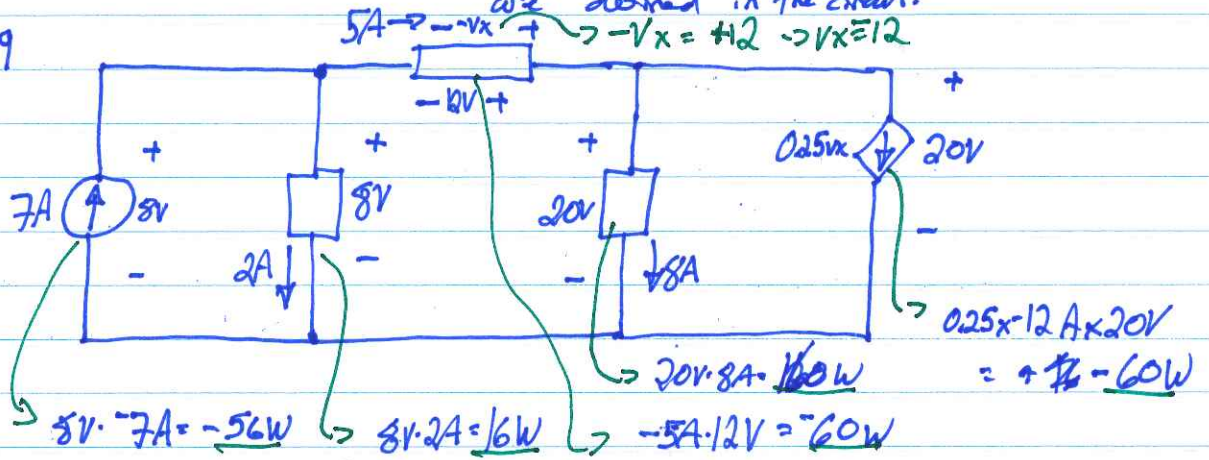

Ohm's Law  $V=RI$  resistance =  $V/A$  ohm =  $\Omega$   
absorbs power

$$P = VI \Rightarrow V = RI$$

$$P = RI^2 = V^2/R$$

Ex. 2.4 500kV, 600MW  $I = \frac{P}{V} = \frac{600 \times 10^6}{500 \times 10^3} = 1.2 \text{ kA}$

$$R = \frac{V}{I} = \frac{500 \times 10^3}{1.2 \times 10^3} = 417 \Omega$$

$$R = \rho \frac{l}{A} \quad l = \text{length} \quad \rho = \frac{R \cdot A}{l} = \frac{(417)(1200)}{l(24 \text{ in})(\frac{5380 \text{ ft}}{\text{in}})(\frac{16 \text{ in}}{\text{ft}})(\frac{2.54 \text{ cm}}{\text{in}})}$$

$$= 500 \mu\Omega \cdot \text{cm}$$



Conductance  $\frac{i}{v} = \frac{1}{R} = G$   $1S = \frac{1}{\Omega}$  siemen

linear resistor ratio of current to voltage

Short circuit - resistance of  $0\Omega$  voltage across  $R = \emptyset$  (current flow)  
 open circuit - has infinite resistance (current is  $\emptyset$ , voltage across part)  
 Wires are perfect short circuits

Chapter 3 - Nodes, Loops + Branches


KCL = Kirchoff's Current Law

sum of currents entering a node is zero  
 charge cannot accumulate at a node

KVL = Kirchoff's Voltage Law

sum of voltages around a closed loop =  $\emptyset$

$$\sum_{n=1}^N v_n = \emptyset$$

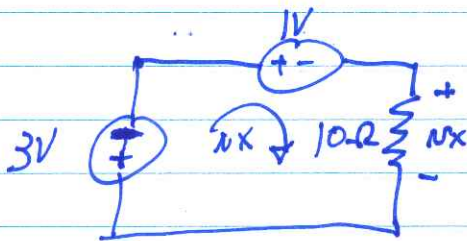


$$+3 + 1V + v_x = 0$$

$$v_x = -4$$

$$+i_x = \frac{v_x}{R} = \frac{-4V}{10}$$

$$= -400mA = i_x$$

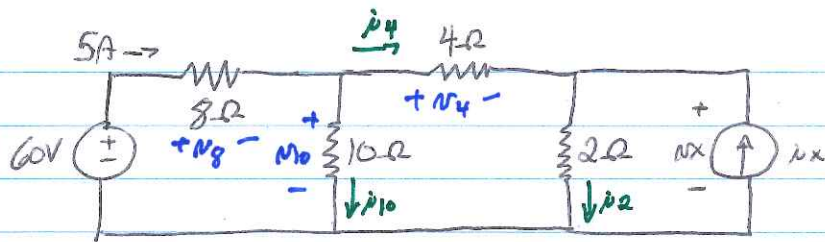

$$i_4 + i_x = i_2$$

$$-60 + v_8 + v_{10} = 0$$

$$v_8 = 5A \cdot 8\Omega = 40V = v_8 \quad \therefore -60 + 40 + v_{10} = 0$$

$$v_{10} = 20V$$

$$i_{10} = 20V / 10\Omega = 2A = i_{10}$$

$$5A = i_{10} + i_4$$

$$i_4 = 3A$$

$$v_4 = i_4 \cdot 4\Omega$$

$$= 3A \cdot 4\Omega = 12V = v_4$$

~~$$5A = i_{10} + i_2 \Rightarrow i_2 = 3A$$~~

~~$$i_4 + i_x = i_2$$~~

$$-v_{10} + v_4 + v_x = 0$$

$$v_x = v_{10} - v_4 = 20 - 12 = 8V = v_x$$