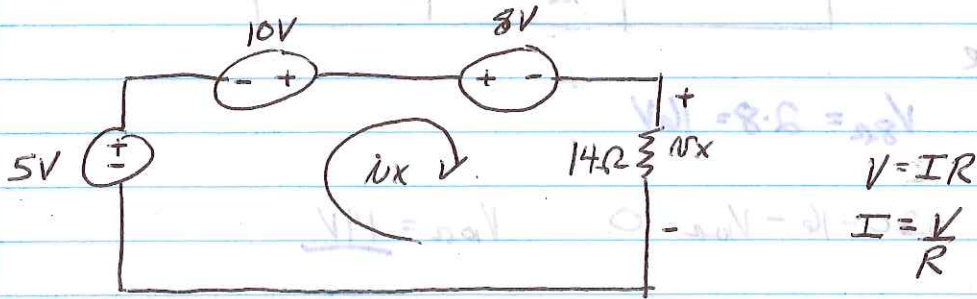


EE 2013 - Fall 2014

Problem 3

09.16.14


KCL:  $\sum_{n=1}^N i_n = 0$       KVL:  $\sum_{n=1}^N v_n = 0$



$5 + 10 - 8 - v_x = 0 \quad \therefore v_x = 7V$

$i_x = \frac{7V}{14\Omega} = 500mA$

Problem 3.3

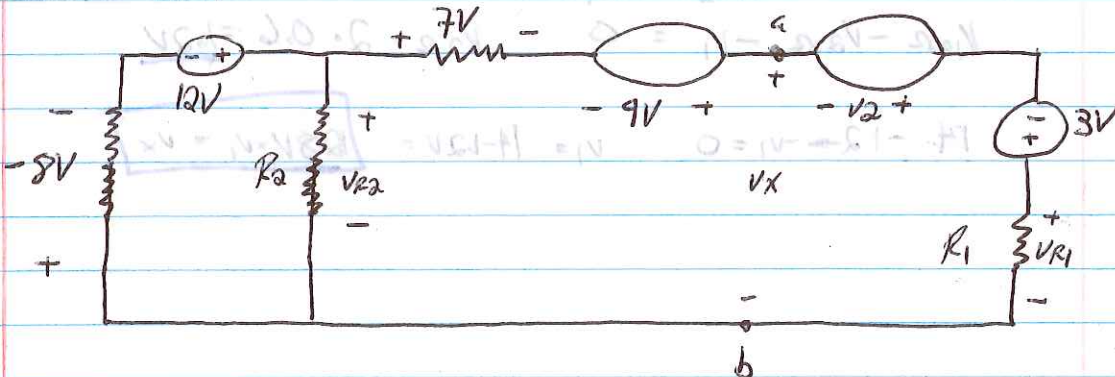

KVL 1st Loop:  $-8 - 12 + v_{R2} = 0 \quad \therefore v_{R2} = 20V$


if  $v_{R1} = 1V$

KVL 2nd Loop:  $20 - 7 + 9 + v_2 + 3 - 1 = 0$

$v_2 + 24 = 0$

$v_2 = -24V$

Practice 3.4

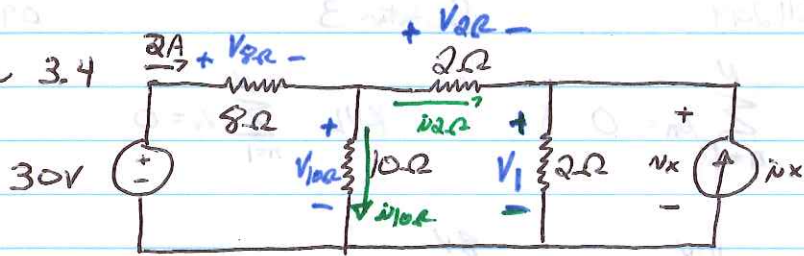

$$V = IR$$

$$V_{8\Omega} = 2 \cdot 8 = 16V$$

$$30 - 16 - V_{10\Omega} = 0 \quad V_{10\Omega} = \underline{14V}$$

$$i_{10\Omega} = \frac{14V}{10\Omega} = 1.4A$$

$$2A - i_{2\Omega} - i_{10\Omega} = 0$$

$$2 - i_{2\Omega} - 1.4 = 0$$


$$i_{2\Omega} = 0.6A$$

$$V_{10\Omega} - V_{2\Omega} - V_1 = 0 \quad V_{2\Omega} = 2 \cdot 0.6 = \underline{1.2V}$$

$$14 - 1.2 - V_1 = 0 \quad V_1 = 14 - 1.2V = \boxed{12.8V = V_1 = v_x}$$

Power  $\sum P_{\text{absorbed}} = \sum P_{\text{supplied}}$

Practice 3.7

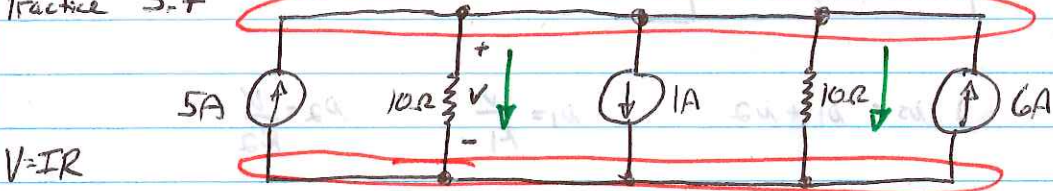


$V=IR$

$$5 - \frac{v}{10} - 1 - \frac{v}{10} + 6 = 0 \quad 10 - \frac{2v}{10} = 0$$

$$10 = \frac{2v}{10} \quad 100 = 2v$$

$v = 50V$

Practice 3.8

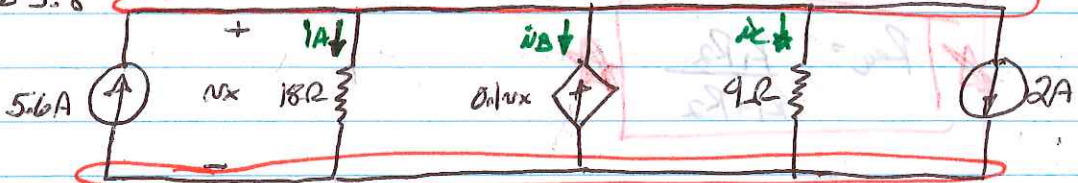

$$5.6 - \frac{vx}{18} + \frac{vx}{10} - \frac{vx}{9} - 2$$

$$3.6 - \frac{vx}{18} = 0$$


$vx = 54$

$$i_A = \frac{54}{18} = 3A = i_A$$

$$i_B = -0.1 \times 54 = -5.4 = i_B$$

$$i_C = \frac{54}{9} = 6A = i_C$$


Resistors in Series

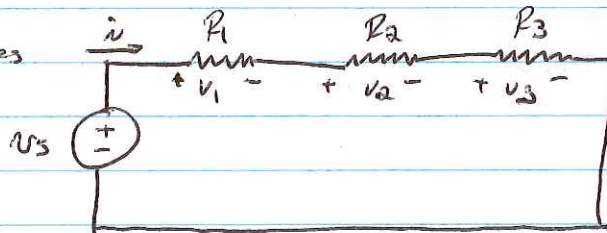

$$v_s = R_1 i + R_2 i + R_3 i \Rightarrow v_s = i (R_1 + R_2 + R_3)$$

$$\frac{V}{I} = R \Rightarrow \frac{v_s}{i} = R_1 + R_2 + R_3$$

### Resistors in Parallel

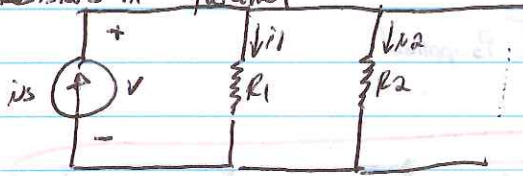

$$i_s = i_1 + i_2$$

$$i_1 = \frac{v}{R_1}$$

$$i_2 = \frac{v}{R_2}$$

$$i_s = \frac{v}{R_1} + \frac{v}{R_2}$$

multiply Both sides by  $R_1 R_2$

$$R_1 R_2 i_s = R_2 v + R_1 v$$

$$i_s R_1 R_2 = v(R_1 + R_2)$$

$$R = \frac{v}{i_s}$$

$$\frac{v}{i_s} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$