

Q4.45

Can use 3 equations for current loop to solve problem. $i_4 = 2A$.
Relationship between common current wires.

SUPER MESH!

Q5.4

- a) ① Short circuit the voltage source and find $i_{x'}$
- ② open circuit the current source and find $i_{x''}$

b) relationship of $i_{x'}$ + $i_{x''}$

c) Change current source to match $i_{x''}$


Q5.17

- ① convert to all voltage sources
- ② Perform KVL, mesh analysis + solve simultaneous equations
- ③ simulate both circuits in LTspice


Q5.18

① Follow steps from lecture

Q5.26

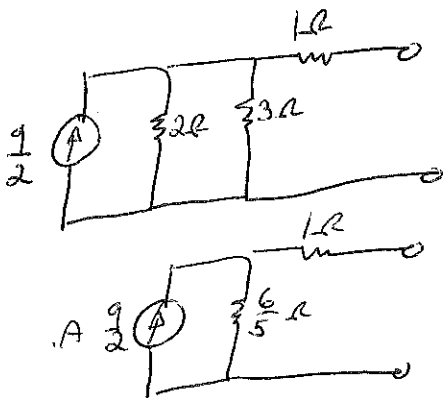

$$\frac{2 \times 3}{5} = \frac{6}{5} R$$

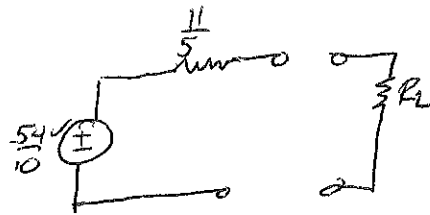

Can plot in MATLAB

Range R_L from 0 to $5R$

$$P[R_L] = \frac{\left[\frac{54}{10} \left[\frac{R_L}{R_L + \frac{11}{5}} \right] \right]^2}{R_L}$$




Q5.32

current meshes

part 2 → Find $i_{ux} = i_{voc}$

Find R_{TH} by shorting voltage & open circuit current source


PRACTICE 5.7

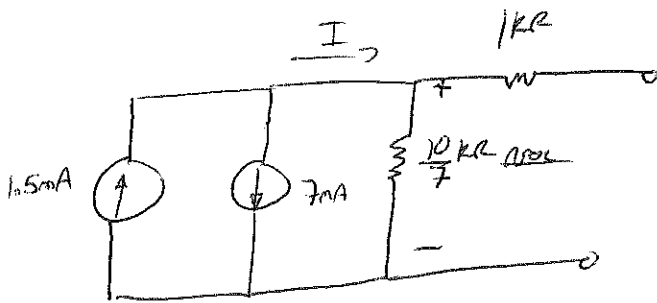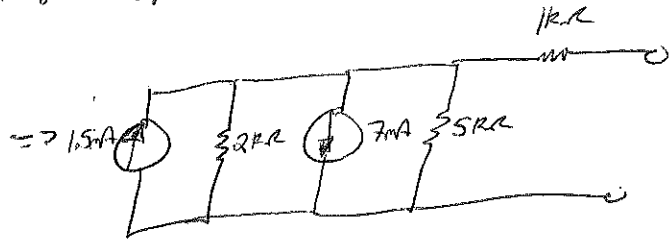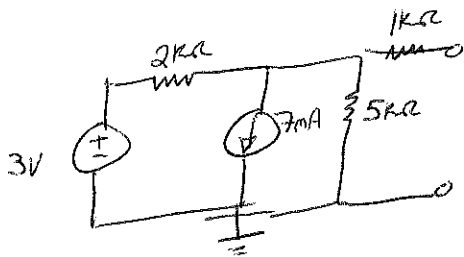

$$v_{oc} = -5.5mA \times \frac{10k\Omega}{7}$$

$$= -7.857V$$

PRACTICE 5.9

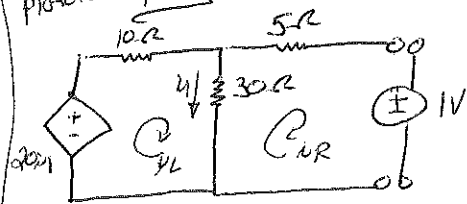

$$-20i_L + 10i_L + 30i_L - 30i_R = 0$$

$$30i_R - 30i_L + 5i_R + 4 = 0$$

$$i_L = i_L - i_R$$

$$-20i_L + 40i_L - 30i_R = 0$$

$$-30i_L + 35i_R = -4$$

$$-i_L + i_L - i_R = 0$$

$$i_R = -50\mu A$$



$-i_R$ flows out of the 4V source

such that $R_{TH} = \frac{4}{50\mu A} = \frac{1}{50 \times 10^{-6}} = 20k\Omega = R_{TH}$

$$I = 1.5mA - 7mA = -5.5mA = I$$


$$\frac{10}{7} + I$$

$$R_{TH} = 2.429k\Omega$$

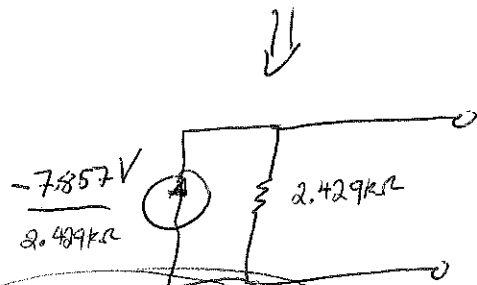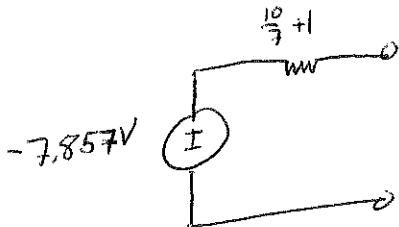

$I_{sc} = -3.235mA$

25.36

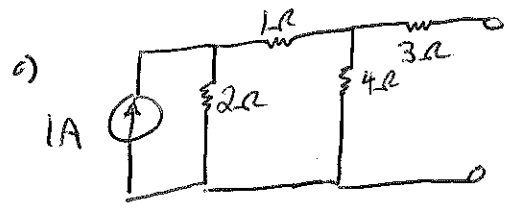

① current won't flow across 3R resistor, so

$$i_{4R} = 1 \times \left(\frac{2}{2+5} \right) = \boxed{\frac{2}{7} \text{ A} = I_{4R}}$$


$$\therefore V_{oc} = V_{4R} = 4 \times \frac{2}{7} = \frac{8}{7} = \boxed{1.143 \text{ V} = V_{oc}}$$

$$R_{oc} = 4 \parallel 3 = \frac{12}{7} \Omega \quad I_{sc} = 1 \text{ A} \times \frac{2}{2+1+\frac{12}{7}} = 424.24 \text{ between } 3 \text{ and } 4$$

$$\therefore I_{sc} = 1 \times \frac{4}{7} = \boxed{242.42 \text{ mA} = I_{sc}}$$

$$\therefore R_{TH} = \frac{V_{oc}}{I_{sc}} = \frac{1.143 \text{ V}}{242.42 \text{ mA}} = 4.715 \Omega$$


b)

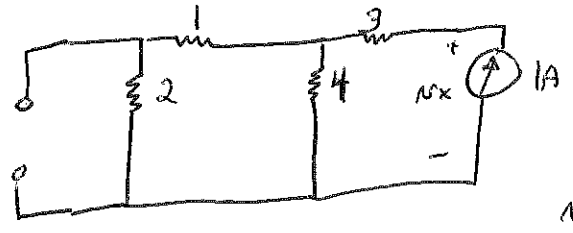

In general $2+3$
 $3 \parallel 4 = \frac{12}{7} + 3 = \frac{33}{7} = 4.715 \Omega$

$$V_x = 1 \text{ A} \times 3 + 4 \parallel 3 = 4.714 \text{ V} \Rightarrow R_{TH} = 4.715 \Omega$$


c)

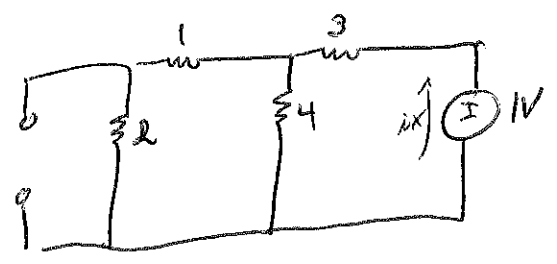

$$I_x = \frac{V}{R} = \frac{1 \text{ V}}{3 \parallel 4} = \frac{7}{33} = I_x$$

$$\therefore R_{TH} = \frac{1 \text{ V}}{\frac{7}{33}} = \boxed{\frac{33}{7} \Omega = R_{TH}}$$

Q5.37.

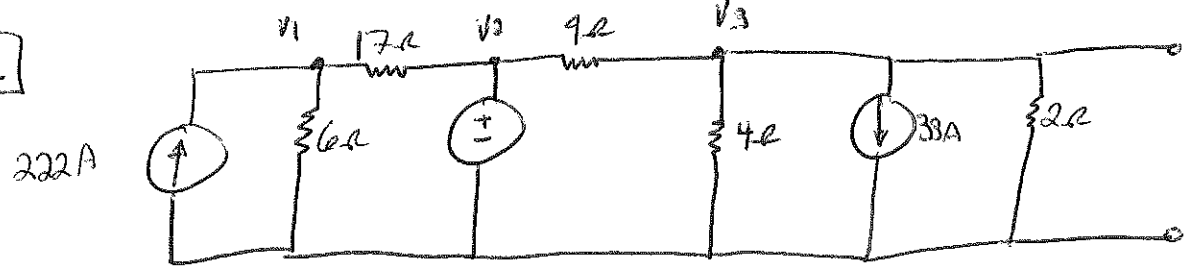

$$0 = -222 + \frac{v_1}{6} + \frac{v_1 - v_2}{17}$$

$v_2 = 20V$
 or

$$0 = \frac{v_3 - v_2}{9} + \frac{v_3}{4} + \frac{v_3}{2} + 33$$

solve for $v_3 = -35.74V$
 $v_{oc} = -35.74$

short terminals + solve isc

$R_{th} = 6 \parallel 7 \quad 9 \parallel 4 \parallel 2 = 16/12$