
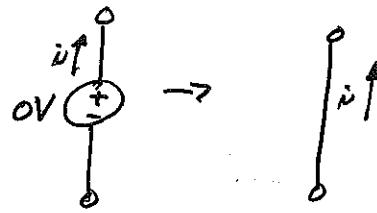



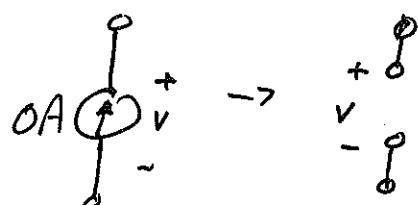
- If voltage drop is 0V, then current flows and acts like a short circuit.



- If no current is flowing, then voltage can appear across terminals.



Practical Voltage Sources:

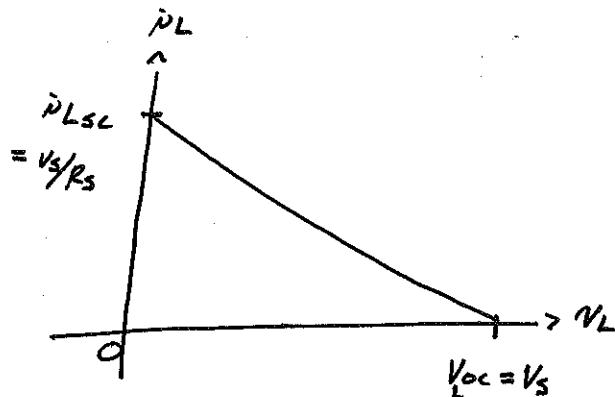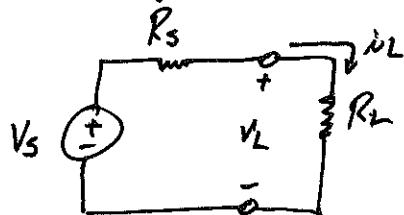

$$V = IR$$



$R_s \rightarrow 0$ $P_{LSC} = \frac{V_s}{R_s}$ $\rightarrow P_{LSC}$ is maximized because there is no resistance.

$R_s \rightarrow \infty$ $P_{LSC} = \frac{V_s}{R_s}$ $\rightarrow P_{LSC}$ goes to 0 since current will not flow through a resistor of ∞ .

Thus, if $R_L = \infty$, no current flows, creating an open circuit ($I_{SC} = 0$) V_{OC} maximized


If $R_L = 0$, then all current flows, creating a short circuit ($V_{OC} = 0$), I_{SC} is maximized.

Practical Current Source:

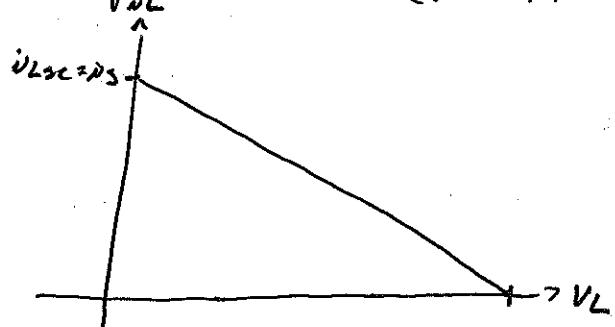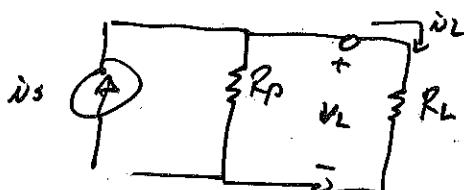


$$R_p \rightarrow \infty \quad (I_s = 0)$$
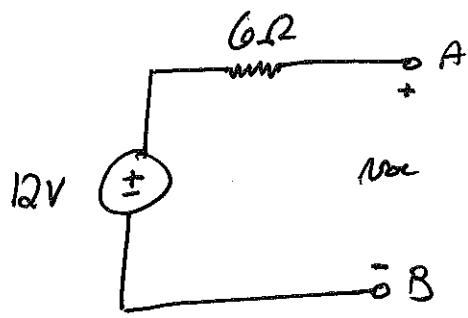
$$R_p \rightarrow 0 \quad (I_s \text{ is maximized})$$



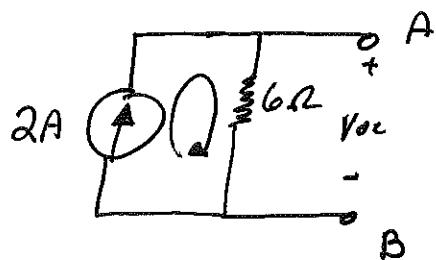
$V_{oc} = ?$ measure voltage from A to B = 12V
 $I_{sc} = ?$ attach short from A to B and measure current flow as
 $I_{sc} = \frac{V_{oc}}{6} = \frac{12V}{6} = 2A = I_{sc}$



$V_{oc} = ?$ measuring V_{oc} from nodes A+B is the same as measuring the voltage across the 6Ω resistor (because in parallel)
 $\therefore V_{oc} = 2A \cdot 6\Omega = 12V = V_{oc}$

$I_{sc} = ?$ put a short between A+B + measure current flow. All 2A will flow through wire.
 $\therefore I_{sc} = 8A$.

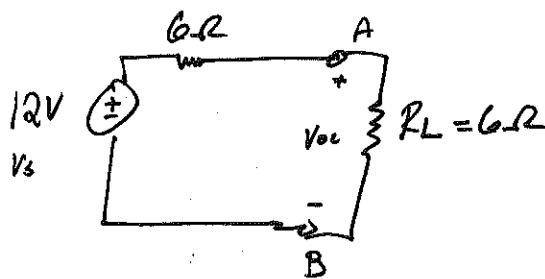See the source transformation / Norton + Thevenin equivalent!



~~Measure V_{RL}~~
 V_{RL} is measured as ~~6V~~ 6V

I_{RL} is measured as 1A

$$V_s \times \frac{R_L}{R_s + R_L} = 6V \Rightarrow V_s \times \cancel{\frac{6}{6+R_s}} = \cancel{6}$$

$$V_s = 6 + R_s$$




~~$I_{RL} = \frac{V_s}{R_L + R_s} = \frac{6}{6+R_s}$~~

$$I_A = \frac{6+R_s}{6+R_s}$$

- ① Remove load + find voltage across it to find V_{TH}
- ② set voltage source to 0V + find equivalent resistance from A to B.

~~$I_{RL} = \frac{V_s}{R_s + R_L}$~~
 ~~$\frac{6}{1} = \frac{V_s \times R_L}{R_s + R_L}$~~
 ~~$6 = \frac{V_s \times R_L}{R_s + R_L}$~~

Delta - WYE

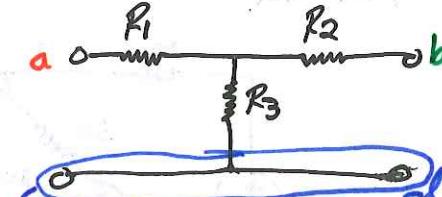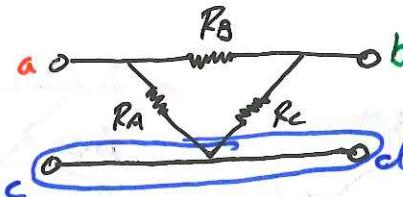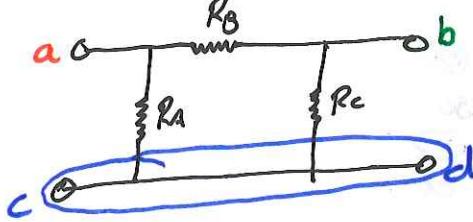

WYE -to- Delta

$$R_A = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2}$$

$$R_B = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}$$

$$R_C = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$




Delta -to- WYE

$$R_1 = \frac{R_A R_B}{R_A + R_B + R_C}$$

$$R_2 = \frac{R_B R_C}{R_A + R_B + R_C}$$

$$R_3 = \frac{R_A R_C}{R_A + R_B + R_C}$$


Exam 2-22. Method 1

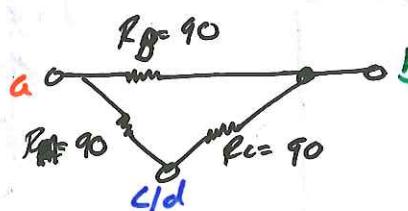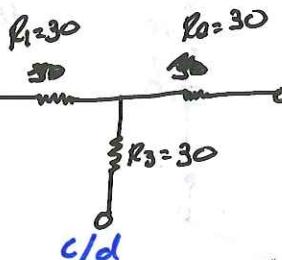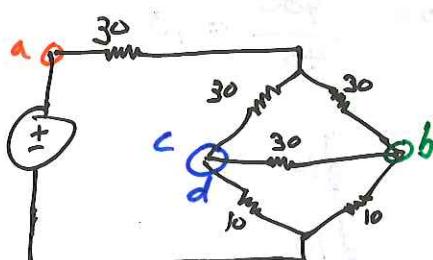

$$R_A = \frac{900 + 900 + 900}{30} = 90$$



$$R_B = \frac{900 + 900 + 900}{30} = 90$$
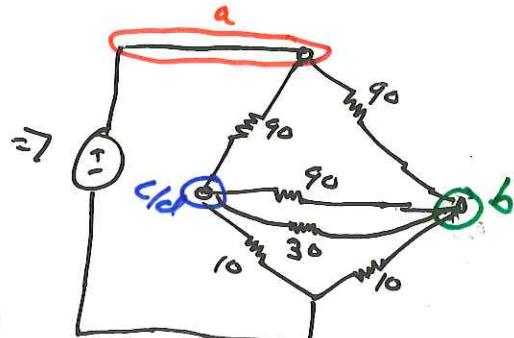
$$R_C = \frac{900 + 900 + 900}{30} = 90$$




Too complicated, too many steps!

Method 2.

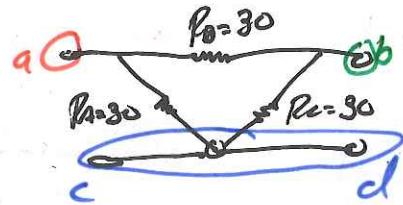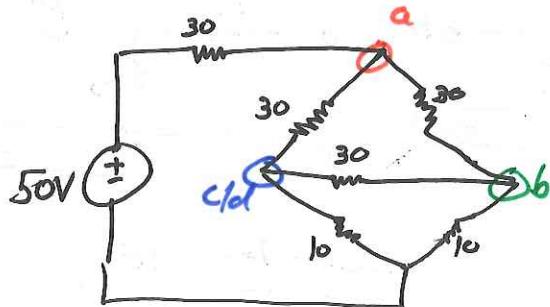


$$R_1 = \frac{30^2}{90} ; R_2 = \frac{30^2}{90} ; R_3 = \frac{30^2}{90}$$

$$R_1 = R_2 = R_3 = 10 \Omega$$

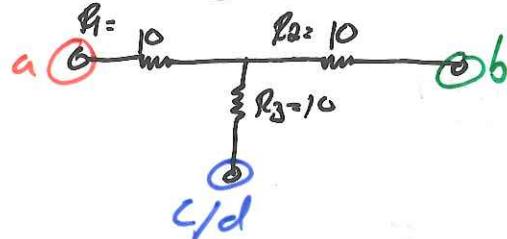


Resultant

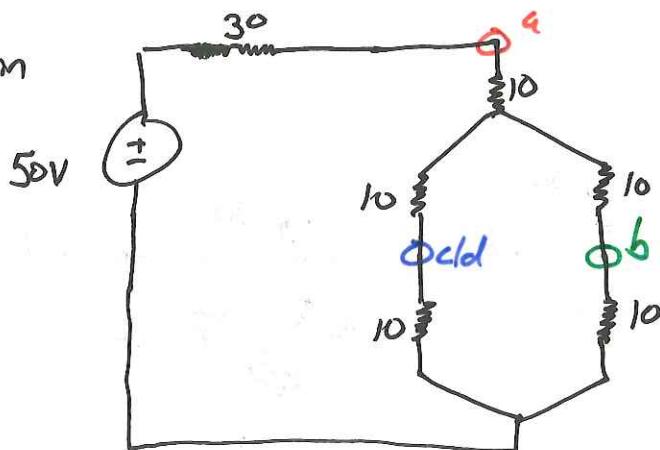

$$10 + 10 = 20$$


$$10 + 10 = 20$$

$$20 // 20 = \frac{400}{40} = 10$$

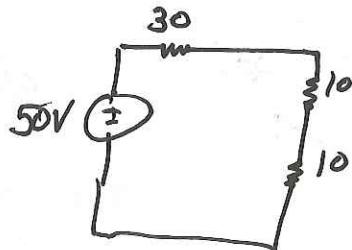


$$R = 30 + 10 + 10 = 50$$


Example

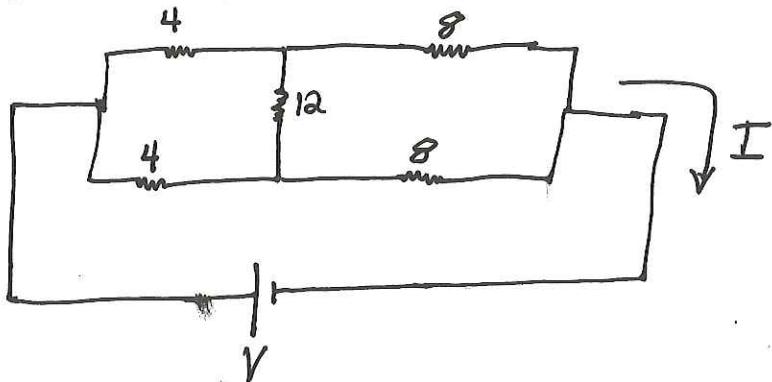

This circuit is Equivalent to :

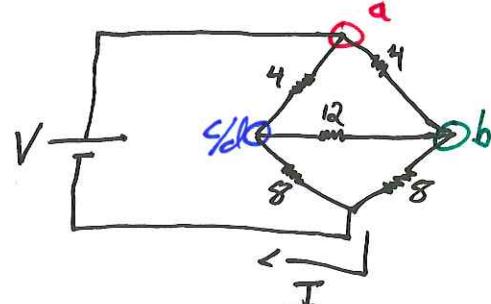

Convert Delta to WYE

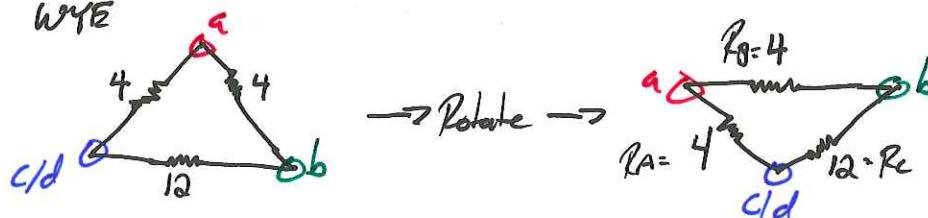

$$R_1 = \frac{(4)(4)}{20} = \frac{4}{5}$$

$$R_2 = \frac{(4)(12)}{20} = \frac{12}{5}$$

$$R_3 = \frac{(4)(12)}{20} = \frac{12}{5}$$

connect this back to the circuit

$$\frac{12}{5} + 8 = \frac{52}{5} ; \quad \frac{52}{5} \parallel \frac{52}{8} \cdot \frac{\left(\frac{52}{8}\right)\left(\frac{52}{8}\right)}{\frac{52}{8} + \frac{52}{8}}$$

$$= \frac{13}{4}$$

$$\frac{13}{4} + \frac{4}{5} = 4.05 \Omega$$

$$\therefore I = \frac{V}{4.05 \Omega}$$

