

EL 2013 - Fall 2014 ~~Rev~~ Revision 8 - 10/28/2014


Active vs. Passive elements. Passive elements cannot supply energy! Active elements can supply energy.

Capacitance is defined by a voltage-current relationship

$$i = C \frac{dv}{dt}$$

Capacitance is measured in Farads
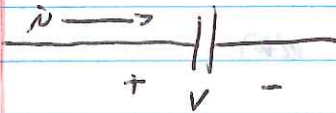
$$1F = \frac{1A \cdot s}{V} = \frac{1C}{V}$$



Charge is stored on a conducting plate. Charge accumulates on the surface of the metal plate and does not enter interior

A capacitor is 2 conducting plates w/ area A separated by distance d and has capacitance $C = \epsilon A/d$

ϵ = permittivity (insulating material)

For air $\epsilon = \epsilon_0 = 8.85 \text{ pF/m}$

Practice 7.1

$$C = 5 \text{ nF}$$

a) $v = -20V$

$$i = C \frac{dv}{dt}$$

$$= (5 \times 10^{-3}) \times -20 \frac{dv}{dt}$$

$$= (5 \times 10^{-3})(0) = 0A$$

b) $v = 2e^{-5t} V$

$$\therefore i = C \frac{dv}{dt} = (5 \times 10^{-3})(-5 \times 2 e^{-5t})$$

$$= -50 \times 10^{-3} A =$$

$$\boxed{-50 \text{ mA} = i}$$

Current-Voltage relationship: $i = C \frac{dv}{dt} \Rightarrow dv = \frac{1}{C} i(t) dt$

Integrate between times t_0 & t_1


$$\int_{v(t_0)}^{v(t_1)} dv = \frac{1}{C} \int_{t_0}^{t_1} i(t') dt'$$

$$v(t_1) - v(t_0) = \frac{1}{C} \int_{t_0}^{t_1} i(t') dt' \quad \therefore v(t) = \frac{1}{C} \int_{t_0}^t i(t') dt' + v(t_0)$$

In many cases, $t_0 = -\infty$ + $V(-\infty) = 0$, such that

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(t') dt'$$

Example 7.2

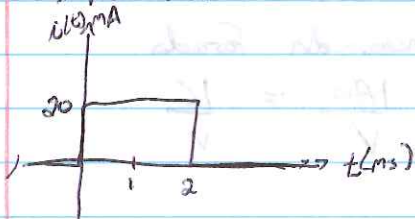

$$C = 5 \mu F$$

$$v(t) = \int_{t_0}^t \frac{1}{C} i(t') dt' + v(t_0)$$

Interval

$$-\infty \leq t \leq 0$$

$$i(t) = 0 \rightarrow v = 0$$

$$0 \leq t \leq 2 \text{ ms}$$

$$\rightarrow v(t) = \int_0^t \frac{1}{C} i(t') dt' + v(0)$$

$$\rightarrow i = 4000t$$


$$2 \text{ ms} \leq t \leq \infty$$

$$\rightarrow v(t) = \int_0^t \frac{1}{C} 20 \times 10^{-3} dt' + 0$$


since current is constant

$$= \frac{1}{(5 \times 10^{-6})} \times t \times 20 \times 10^{-3} \Big|_0^{2 \times 10^{-3}} = 8 \text{ V} = 4000t = v(t)$$

$$v(t) = \begin{cases} 0 & \text{for } -\infty \leq t \leq 0 \\ 4000t & \text{for } 0 \leq t \leq 2 \text{ ms} \\ 0 + (4000)(2 \text{ ms}) = 8 \text{ V} & \text{for } 2 \text{ ms} \leq t \leq \infty \end{cases}$$

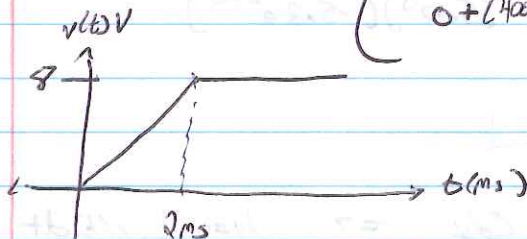

Practice 7.2

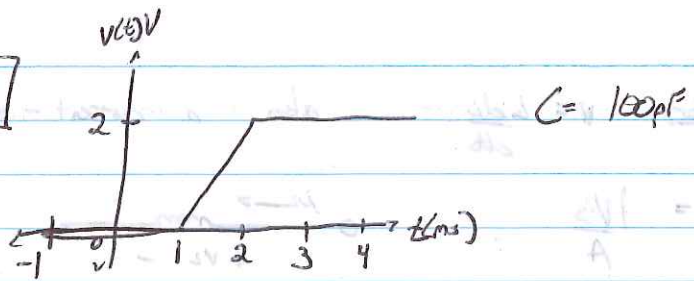


$i = C \frac{dv}{dt}$

Interval $-\infty$ to 1ms $\frac{dv}{dt} = 0 \Rightarrow i = 0$

Interval 1ms to 2ms $\frac{dv}{dt} = \frac{2\text{V}}{1 \times 10^{-3}\text{s}} = 2000 \text{ V/s}$

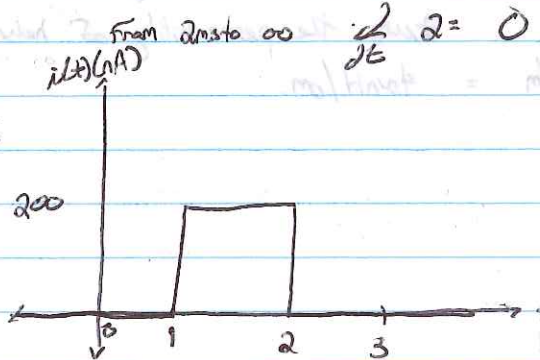$i = 100 \times 10^{-12} \text{ F} \times 2000 \text{ V/s} = 200 \times 10^{-9} \text{ A} = 200 \text{ nA}$



Energy storage $P = V \cdot I = C v \frac{dv}{dt}$

$\int \text{Power} = \text{Energy} \quad P = C v \frac{dv}{dt}$

$\int_{t_0}^t p dt' = C \int_{t_0}^t v \frac{dv}{dt'} dt'$

$P = \frac{dE}{dt} = C v \frac{dv}{dt} \rightarrow dE = C v dv$


$\int_{E(t_0)}^{E(t)} dE = \int_{v(t_0)}^{v(t)} C v dv \rightarrow E_C(t) - E_C(t_0) = \frac{1}{2} C [v(t)^2 - v(t_0)^2]$

$\therefore E_C(t) - E_C(t_0) = \frac{1}{2} C [v(t)^2 - v(t_0)^2]$

If $E_C(t_0) = 0$ then $E_C(t) = \frac{1}{2} C v(t)^2 = \frac{1}{2} C v^2$

Inductor $V = L \frac{di}{dt}$ also a current-voltage relationship

$$1H = \frac{1Vs}{A}$$

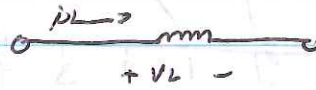

winding wire into a coil. $\#$ of turns affects the current

in general $L = \mu N^2 \frac{A}{l}$ where N = $\#$ of complete turns of wire

A is cross sectional area

l is axial length of ~~inductor~~ ^{the helix}


μ is the permeability of helix material

~~is~~ in air

$$\mu = \mu_0 = 4\pi \times 10^{-7} H/m = 4\pi nH/cm.$$

$$V = L \frac{di}{dt}$$

Example 7.4

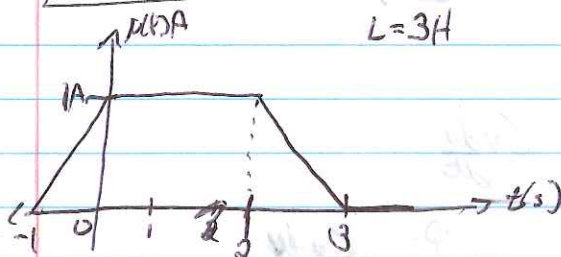

Interval

$-\infty$ to -1 current = 0, $V = 0$


$$-1$$
 to $0 \quad L \cdot \frac{di}{dt} = L \cdot 1 = 3 \cdot \frac{1}{1} = 3V$

$$= 3V$$

0 to $2 \quad 3 \cdot \frac{di}{dt} = 0$ constant current
= constant voltage.

$$2$$
 to $3 \rightarrow 3 \cdot \frac{-1}{1} = -3V$

3 to $\infty \rightarrow = 0$ constant current = 0V

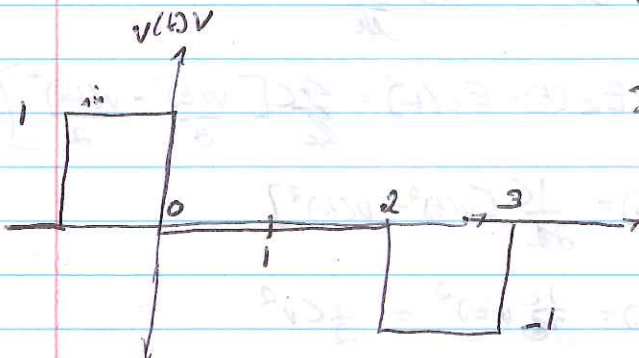

Practise 7.4

$L = 200\text{mH}$

$V_L = L \frac{di}{dt}$

$\frac{di}{dt}$ is the rate of change of the current which is the derivative of the current or slope of the line over an interval.

slope = $\frac{\text{rise}}{\text{run}}$ = $\frac{\text{change in } y}{\text{change in } x}$

For Figure 7.13

Interval
A to B

Voltage

$-\infty$ to -3ms no current $V = 0\text{V}$


-3ms to 1ms = $200\text{mH} \times \frac{2 \text{ A}}{1 \text{ s}} = 200 \times 10^{-3} \times 2 = 400\text{mV}$

1ms to 3ms = $200\text{mH} \times \frac{2 \text{ A}}{2 \text{ s}} = 200 \times 10^{-3} \times 1 = 200\text{mV}$

3ms to 6ms = $200\text{mH} \times \frac{4 \text{ A}}{3 \text{ s}} = -\frac{800}{3} \text{ mV} = -266.67\text{mV}$

- a) $V_L(0) = 0.4\text{V}$
- b) $V_L(2\text{ms}) = 0.2\text{V}$
- c) $V_L(6\text{ms}) = 0.266\text{V}$

Example 7.5

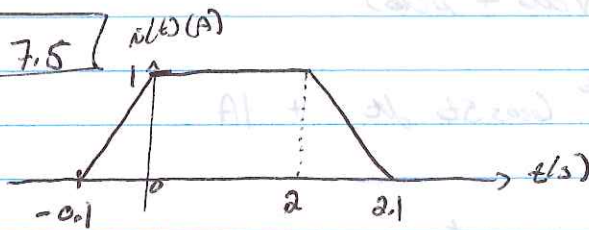

$L = 3\text{H}$

$V = L \frac{di}{dt}$

Interval

Voltage

$-\infty \leq t \leq -0.1$

DC current $\rightarrow V = 0$

$-0.1 \leq t \leq 0$

$\frac{d}{dt} 0 - 1 = 10^3 \times 3\text{H} = 30\text{V}$

$0 \leq t \leq 2$



DC current $\rightarrow V = 0$

$2 \leq t \leq 2.1$

$3\text{H} \cdot \frac{d}{dt} 1 - 0 = 3 \times \frac{-1}{0.1} = 3 \times 10 = -30\text{V}$

$2.1 \leq t \leq \infty$

DC current $V = 0$

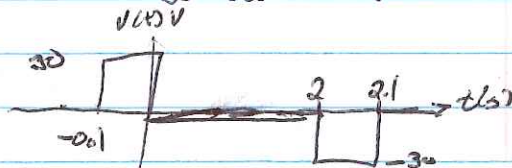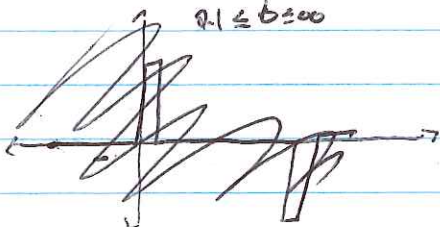

Integral relationship

$$v = L \frac{di}{dt}$$

$$di = \frac{1}{L} v dt$$

$$\int_{i(t_0)}^{i(t)} di = \frac{1}{L} \int_{t_0}^t v(t') dt'$$

$$i(t) - i(t_0) = \frac{1}{L} \int_{t_0}^t v(t') dt'$$

$$\rightarrow i(t) = \frac{1}{L} \int_{t_0}^t v(t') dt' + i(t_0)$$

$$\therefore i(t) = \frac{1}{L} \int_{t_0}^t v dt' + i(t_0)$$

Example 7.6 $L = 2H$ $v = 6 \cos 5t$

$\therefore i(t = -\pi/2) = 1A$ make $t_0 = -\pi/2$ $i(t_0) = 1A$

$$\therefore i(t) = \frac{1}{L} \int_{t_0}^t v dt + i(t_0)$$

$$= \frac{1}{2} \int_{t_0}^t 6 \cos 5t dt + 1A$$

$$\therefore \frac{1}{2} \left[\frac{6}{5} \sin(5t) \right]_{t_0}^t + 1A$$

$$= \frac{1}{2} \left[\frac{6}{5} \sin(5t) - \frac{6}{5} \sin\left(5 \times \frac{-\pi}{2}\right) \right] + 1A$$

$$= \frac{3}{5} \sin(5t) - \left(-\frac{3}{5}\right) + 1 \rightarrow \boxed{i(t) = \frac{3}{5} \sin(5t) + 1.6 A}$$

Practise 7.6 $L = 100 \text{ mH}$ $v_L = 2e^{-3t} \text{ V}$

$i_L(-0.5) = 1 \text{ A}$ $t_0 = -0.5$ $i_L(t_0) = 1 \text{ A}$

$$i_L(t) = \frac{1}{L} \int_{t_0}^t 2e^{-3t} dt + i_L(t_0)$$

$$i_L(t) = \frac{1}{100 \times 10^{-3}} \times \frac{-2}{3} e^{-3t} \Big|_{t_0}^t + 1 \text{ A}$$

$$\therefore i_L(t) = \frac{20}{36} \left[e^{-3t} \Big|_{-0.5}^t \right] + 1 \text{ A}$$

$$= \frac{20}{36} \left[e^{-1.5} - e^{-3t} \right] = \frac{20}{3} e^{-3t} + 30.8779 \text{ A} = i_L(t)$$

Energy storage $p = v \cdot i = L i \frac{di}{dt}$

$$\# \quad p = \frac{dE}{dt} = L i \frac{di}{dt} \quad dE = L i di$$

$$\int_{t_0}^t dE = L \int_{i(t_0)}^{i(t)} p di \rightarrow E_L(t) - E_L(t_0) = L \left[\frac{i(t)^2}{2} - \frac{i(t_0)^2}{2} \right]$$

$$\therefore E_L(t) - E_L(t_0) = \frac{L}{2} [i(t)^2 - i(t_0)^2]$$

$$\text{if } E_L(t_0) = 0, \quad E_L(t) = \frac{1}{2} L i^2$$

Example

$$\text{if } C = 12 \mu\text{F}$$

$$+ v_C(2) = 10 \text{ V}, v_C(t_0) = 4 \text{ V}, w_C(t_0) = 2 \text{ nJ}$$

what is $w_C(t)$ at $t = 2 \text{ s}$

$$\text{Eq. 3 page 202, } w_C(t) - w_C(t_0) = \frac{1}{2} C [v_C(t)^2 - v_C(t_0)^2]$$

$$\therefore w_C(t) = \frac{1}{2} C [v_C(t)^2 - v_C(t_0)^2] + w_C(t_0)$$

$$= \frac{1}{2} (12 \times 10^{-12}) [(10^2) - (4^2)] + 2 \text{ nJ}$$

$$= 2.504 \text{ nJ}$$

$$V^{(2)} = 0 = V \text{ (total value of debt and equity)}$$

$$A = (1+r)^2 \text{ (debt)} + A - (1+r)^2 \text{ (equity)}$$

$$A(1+r)^2 - A(1+r)^2 = 0 \Rightarrow A = 0$$

$$A = \frac{0}{1 - (1+r)^{-2}} = 0$$

$$A = \frac{0}{1 - (1+r)^{-2}} = 0$$

$$\text{Total amount} = \frac{0}{1 - (1+r)^{-2}} = 0$$

$$A = 0$$

$$A = 0$$

$$\left[\frac{0}{1 - (1+r)^{-2}} \right] = 0$$

$$\left[\frac{0}{1 - (1+r)^{-2}} \right] = 0$$

$$0 = 0$$

$$0 = 0$$

$$A = 0$$

$$\left[\frac{0}{1 - (1+r)^{-2}} \right] = 0$$

$$\left[\frac{0}{1 - (1+r)^{-2}} \right] = 0$$

$$A = 0$$

$$A = 0$$

⊕